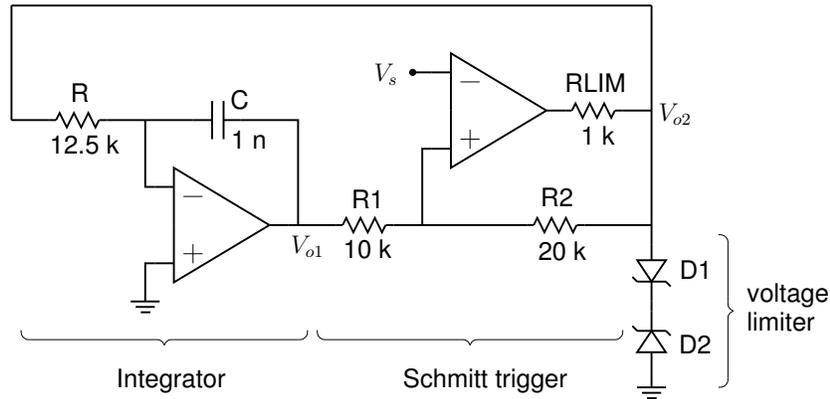


## opamp\_osc\_1.sqproj



Shown in the figure is an oscillator circuit which produces a triangle wave at  $V_{o1}$  and a square wave at  $V_{o2}$ . The Zener diodes serve to limit the output voltage to  $\pm(V_Z + V_D)$ .

### Exercise Set

1. For the component values given in the figure and with  $V_s = 0 V$ ,
  - (i) Sketch the  $V_o$  versus  $V_i$  characteristic for the Schmitt trigger.
  - (ii) Find the relationship between  $V_i$  and  $V_o$  for the integrator.
  - (iii) What is the frequency of the oscillations?
  - (iv) What are the minimum and maximum values of  $V_{o1}(t)$ ?
2. Repeat 1 for  $V_s = 2 V$ .
3. Repeat 1 for  $V_s = -2 V$ .
4. What is the purpose of the resistor RLIM?

Verify your results with simulation.

### References

1. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.
2. J. Millman and A. Grabel, *Microelectronics*, McGraw-Hill, 1988.

3. A. S. Sedra, K. C. Smith, and A. .N. Chandorkar, *Microelectronic Circuits*, Oxford University Press, 2004.