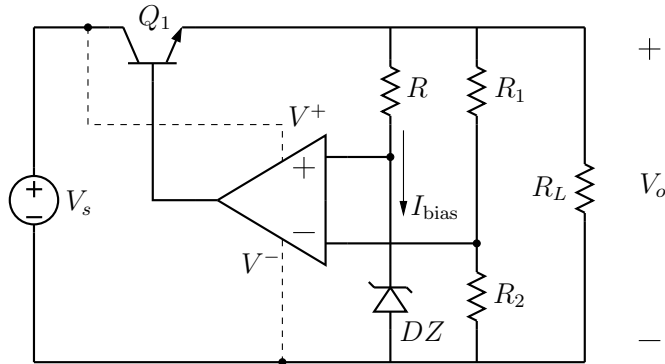


## opamp\_regulator\_1.sqproj



The purpose of a voltage regulator is to provide a constant DC voltage to the load in spite of variations in the input DC voltage or in the load. In the circuit shown in the figure, the “control element” ( $Q_1$ ) is in series with the load  $R_L$ , and this configuration is therefore called a “series mode regulator.” The Zener diode provides a reference voltage. The resistor  $R$  is selected in order to bias the Zener diode:

$$I_{\text{bias}} = \frac{V_o - V_Z}{R}. \quad (1)$$

Assuming the Op Amp to be operating in the linear region, we have

$$V_+ \approx V_- \Rightarrow V_Z = \frac{R_2}{R_1 + R_2} V_o, \quad (2)$$

$$\text{i.e., } V_o = V_Z \left(1 + \frac{R_1}{R_2}\right). \quad (3)$$

Note that the above equation does not involve the input voltage  $V_s$ . If  $V_s$  changes from  $V_s$  to  $(V_s + \Delta V_s)$ , the change  $\Delta V_s$  gets absorbed in the  $V_{CE}$  of the transistor. In that sense, the output is isolated from the input by the transistor.

### Exercise Set

1. For  $V_s = 15\text{ V}$ ,  $V_Z = 2.9\text{ V}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R = 5\text{ k}\Omega$ ,  $R_L = 100\ \Omega$ , what is the expected value of  $V_o$ ?
2. Vary  $V_s$  from  $13\text{ V}$  to  $16\text{ V}$ , keeping the other parameters the same as before, and obtain a plot of  $V_o$ ,  $V_{BE}$ ,  $V_+$ ,  $V_-$  versus  $V_s$  by simulation.

3. For a fixed value of  $V_s$  (say,  $15\text{ V}$ ), vary  $R_L$  from  $100\ \Omega$  to  $10\text{ k}\Omega$ , and obtain a plot of  $V_o$ ,  $V_{BE}$ ,  $V_+$ ,  $V_-$  versus  $\log R_L$  by simulation.