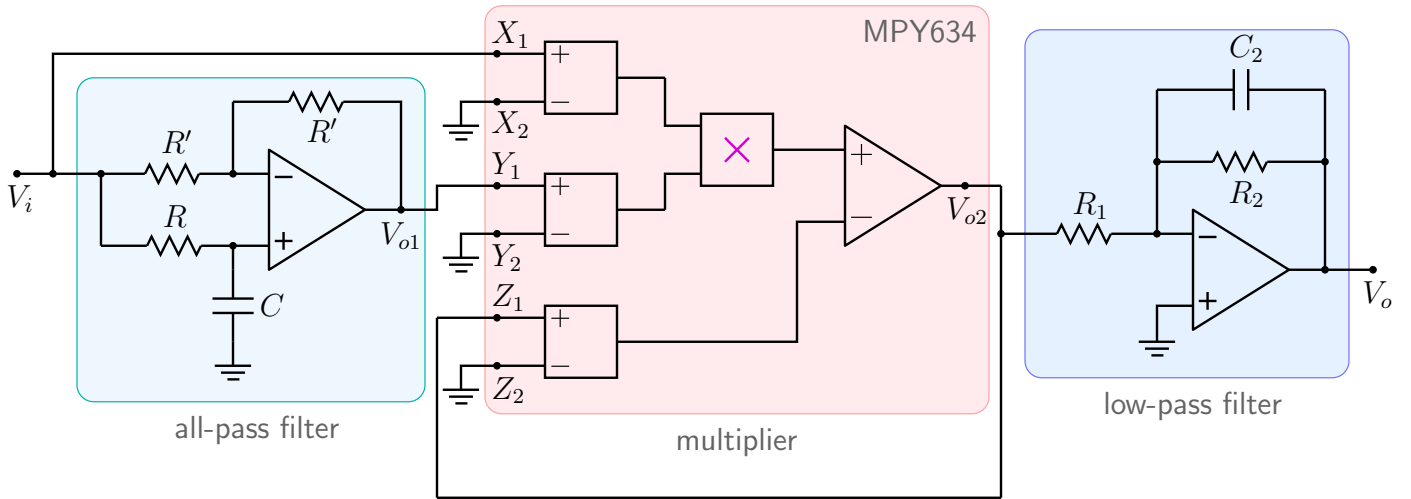


phase_detector_1.sqproj



Shown in the figure is a circuit which produces an output voltage proportional to $\cos \alpha$, where α is the phase difference between two voltages. An all-pass filter is used to generate a phase-shifted version (V_{o1}) of the input voltage V_i , and these two voltages (V_i and V_{o1}) are used as the test voltages. In a simulation exercise, it is possible to bypass this step and directly apply two voltages with the same amplitude and different phase angles; however, the set-up shown here is advantageous when an experimental implementation is desired. The circuit operation can be explained as follows.

The output of the all-pass filter is given by

$$V_{o1}(s) = \frac{1 - sRC}{1 + sRC} V_i(s),$$

which means that $V_{o1}(s)$ has the same amplitude as $V_i(s)$, but a different phase. If $V_i(t) = V_m \sin \omega t$, V_{o1} is given by $V_{o1}(t) = V_m \sin(\omega t + \alpha)$ where $\alpha = -2 \tan^{-1}(\omega RC)$.

The output of the multiplier is given by,

$$\begin{aligned} V_{o2} &= \frac{1}{SF} \times V_i(t) \times V_{o1}(t) \\ &= \frac{1}{SF} \times V_m \sin \omega t \times V_m \sin(\omega t + \alpha) \\ &= \frac{1}{2} \frac{V_m^2}{SF} \times [\cos \alpha - \cos(2\omega t + \alpha)], \end{aligned}$$

where SF is the scaling factor of the multiplier and is equal to 10 V (unless it is changed by the user with an external arrangement).

The low-pass filter is meant to filter out the 2ω component of $V_{o2}(t)$, giving

$$V_o = -\frac{R_2}{R_1} \frac{V_m^2}{2SF} \times \cos \alpha \equiv -k \cos \alpha.$$

Exercise Set

1. For $R' = 1 \text{ k}$, $C = 0.1 \mu\text{F}$, $R = 1 \text{ k}$, $R_1 = 10 \text{ k}$, $R_2 = 47 \text{ k}$, $C_2 = 1 \mu\text{F}$, $V_m = 1 \text{ V}$, $f = 1 \text{ kHz}$,
 - (a) What is the phase difference α between $V_i(t)$ and $V_{o1}(t)$?
 - (b) What is the corner frequency of the low-pass filter?
 - (c) What is V_o ?
 - (d) Simulate the circuit and compare the simulation results with your answers.
2. Repeat the above calculations for $R = 2.2 \text{ k}$, 4.7 k , and 10 k .