

precision_full_wave.sqproj

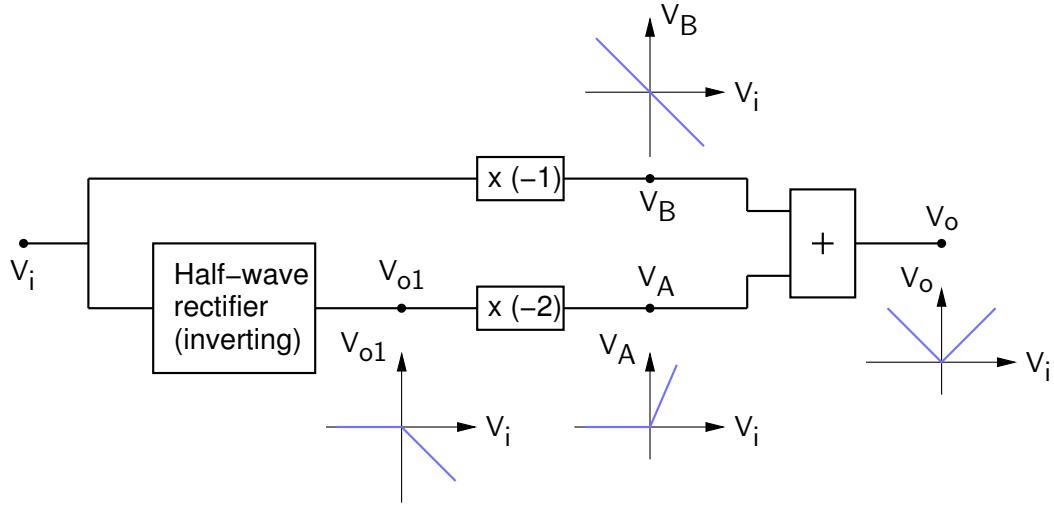


Figure 1: Block diagram of a precision full wave rectifier.

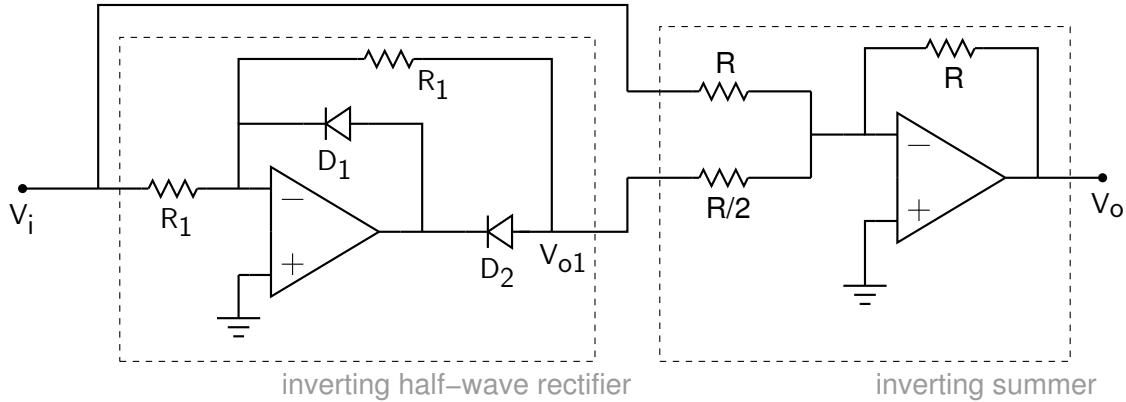


Figure 2: Op Amp based implementation of the circuit in Fig. 1.

A precision half wave rectifier and an Op Amp summer can be used to build a precision full wave rectifier, as shown in the block diagram of Fig. 1. Schematic diagrams showing the relationship between the output of a block with respect to the input voltage¹ is also shown. Fig. 2 shows the implementation of the block diagram with Op Amp circuits, viz., a precision half wave rectifier and a weighted summer.

¹Note that this is the input to the full wave rectifier, not the input to that particular block.

Exercise Set

1. Explain how the implementation in Fig. 2 corresponds to the block diagram of Fig. 1.
2. Run the simulation and verify that the circuit performs precision full wave rectification.

References

1. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.
2. A. S. Sedra, K. C. Smith, and A. N. Chandorkar, *Microelectronic Circuits: Theory and Applications*, Fifth edition, Oxford University Press, 2009.
3. J. Millman and A. Grabel, *Microelectronics*, McGraw-Hill, 1988.