

**Transient and Frequency Response Simulation of Fifth-Order
Chebyshev Low-pass Biphase Switched-Capacitor Circuit (Cascade Approach)**
(Prepared by: Rajesh A. Thakker, Govt. Engg. College, Chandkheda, Gandhinagar,
Email id: rathakker2008@gmail.com)

Circuit file: sc_lpf_5th_1.in

Fig.1 shows the 5th-order Chebyshev low-pass filter (cascade approach) switched capacitor circuit with all parameters. This circuit is simulated here in both domains, Frequency and Time. It is viewed as a connection of many commonly found SC blocks, namely toggle switched inverter (sc_tsi_1), switched resistor (sc_res_1), floating capacitor (sc_float_cap) and switched-capacitor opamp (sc_opamp1).

One such block is shown in Fig. 2 with its Time-domain (a) and Frequency-domain (b) equivalent circuits. As shown in the Fig.2, time-domain circuit is two-port (don't consider the nodes connected with low-value resistance (Rdl)), where as its frequency-domain (z-domain) equivalent circuit consists of four ports. Unused ports or nodes are connected with low-value resistance (Rdl) in Time-domain and High-value resistance (Rdh) in frequency-domain to avoid matrix to become singular.

All commonly found blocks are described as compound elements in SEQUEL with separate time-domain and frequency-domain description. Frequency-domain description assumes ideal elements and equal phase intervals. Time-domain description permits study of non-ideal elements and unequal phase intervals.

The simulated transient and frequency domain response are shown in Fig. 3 and Fig. 4 respectively. The approach utilized here to generate frequency response for switched-capacitor networks is such that it provides frequency response (magnitude and phase responses) for even and odd phases separately. If both of them are nonzero for the frequency-range of interests then they should be combined together by adding real parts of both phase and the same for imaginary parts. Now both terms should added after squared and square root should be calculated. Now it could be converted to gain.

1. Circuit Block:

```
title: 5th order chebyshev (cascade) low pass filter
```

```
greal tc=0.05m roff=1e12 rinop=1e12 ron=1 av=1e5 tcby2=0.025m
```

```
* Define a global parameter tc (clock period), roff and ron (switch off and on  
* resistances), rin (input resistance) and av (voltage gain) of op-amp and  
* tcby2.
```

```
begin_circuit
```

```
  eelement type=vsrcac p=a n=g a=1 f_hz=600 t0=0 phi=0
```

```
* This element produces sine-wave source with frequency 600 Hz.
```

```
  eelement name=srcl type=sc_source_2 vo_e=1e vo_o=1o g=g
```

```
+   aux1=a tc=tcby2 dt=1u s_2=25.0u
```

```
+   tau_1=25.0u tau_2=25.0u
```

* This element samples the sinewave generated above at one-half of clock frequency for even and odd phase and it also constructs the frequency-domain representation for both even and odd phase sampled sinewave.

```
eelement type=sc_tsi_1
+   vi_e=1e vi_o=1o vo_e=2e vo_o=2o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.0909p tc=tc
```

* This element implements toggle switched inverter.

```
eelement type=sc_res_1
+   vi_e=2e vi_o=2o vo_e=3e vo_o=3o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.0909p tc=tc
```

* This element implements switched resistor.

```
eelement type=sc_float_cap
+   vi_e=2e vi_o=2o vo_e=3e vo_o=3o g=g
+   c=1p tc=tc
```

* This element implements floating capacitor.

```
eelement type=sc_res_1
+   vi_e=3e vi_o=3o vo_e=4e vo_o=4o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.2058p tc=tc
```

* This element implements switched resistor.

```
eelement type=sc_float_cap
+   vi_e=4e vi_o=4o vo_e=5e vo_o=5o g=g
+   ron=ron roff=roff c=1p tc=tc
```

* This element implements floating capacitor.

```
eelement type=sc_tsi_1
+   vi_e=5e vi_o=5o vo_e=6e vo_o=6o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.2058p tc=tc
```

* This element implements toggle switched inverter.

```
eelement type=sc_float_cap
+   vi_e=6e vi_o=6o vo_e=7e vo_o=7o g=g
+   ron=ron roff=roff c=1p tc=tc
```

* This element implements floating capacitor.

```
eelement type=sc_res_1
+   vi_e=7e vi_o=7o vo_e=4e vo_o=4o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.2058p tc=tc
```

* This element implements switched resistor.

```
eelement type=sc_res_1
+   vi_e=7e vi_o=7o vo_e=6e vo_o=6o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.1472p tc=tc
```

* This element implements switched resistor.

```
eelement type=sc_res_1
+   vi_e=7e vi_o=7o vo_e=8e vo_o=8o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.3123p tc=tc
```

* This element implements switched resistor.

```
eelement type=sc_float_cap
+   vi_e=8e vi_o=8o vo_e=9e vo_o=9o g=g
+   c=1p tc=tc ron=ron roff=roff
```

* This element implements floating capacitor.

```
eelement type=sc_tsi_1
+   vi_e=9e vi_o=9o vo_e=10e vo_o=10o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.3123p tc=tc
```

* This element implements toggle switched inverter.

```
eelement type=sc_float_cap
+   vi_e=10e vi_o=10o vo_e=11e vo_o=11o g=g
+   c=1p tc=tc ron=ron roff=roff
```

* This element implements floating capacitor.

```
eelement type=sc_res_1
+   vi_e=11e vi_o=11o vo_e=8e vo_o=8o g=g phi_e=phi_e phi_o=phi_o
+   ron=ron roff=roff c=0.3123p tc=tc
```

* This element implements switched resistor.

```
eelement type=sc_float_cap
+   vi_e=11e vi_o=11o vo_e=8e vo_o=8o g=g
+   c=0.18p tc=tc ron=ron roff=roff
```

* This element implements floating capacitor.

```
eelement name=op1 type=sc_opamp1 vi_ep=g vi_em=2e vi_op=g
+   vi_om=2o vo_eo=3e vo_oo=3o gnd=g
+   rin=rinop rout=0 av=av
```

* Above statement implements switched capacitor op-amp.

* This op-amp consists of two op-amps one for each phase.

```
eelement name=op2 type=sc_opamp1 vi_ep=g vi_em=4e vi_op=g
+   vi_om=4o vo_eo=5e vo_oo=5o gnd=g
+   rin=rinop rout=0 av=av
```

* Above statement implements switched capacitor op-amp.

* This op-amp consists of two op-amps one for each phase.

```
eelement name=op3 type=sc_opamp1 vi_ep=g vi_em=6e vi_op=g
+   vi_om=6o vo_eo=7e vo_oo=7o gnd=g
```

```

+     rin=rinop rout=0 av=av
* Above statement implements switched capacitor op-amp.
* This op-amp consists of two op-amps one for each phase.

     eelement name=op4 type=sc_opamp1 vi_ep=g vi_em=8e vi_op=g
+     vi_om=8o vo_eo=9e vo_oo=9o gnd=g
+     rin=rinop rout=0 av=av

* Above statement implements switched capacitor op-amp.
* This op-amp consists of two op-amps one for each phase.

     eelement name=op5 type=sc_opamp1 vi_ep=g vi_em=10e vi_op=g
+     vi_om=10o vo_eo=11e vo_oo=11o gnd=g
+     rin=rinop rout=0 av=av

* Above statement implements switched capacitor op-amp.
* This op-amp consists of two op-amps one for each phase.

     delement type=clock a=phi_e i0=0 t1=25.1u t2=24.9u t0=0
     delement type=clock a=phi_o i0=1 t1=24.9u t2=25.1u t0=0

* These two statements generate non-overlapping clock signal to make the
* switches on and off in even and odd phases.

     refnode=g

* Node g is defined as the reference node for node voltages.

     outvar:
+     va=nodev_of_a vle=nodev_of_1e vlo=nodev_of_1o
+     va_ac=nodev_ac_of_a vle_ac=nodev_ac_of_1e vlo_ac=nodev_ac_of_1o
+     v3e=nodev_of_3e v3o=nodev_of_3o
+     v3e_ac=nodev_ac_of_3e v3o_ac=nodev_ac_of_3o
+     v7e=nodev_of_7e v7o=nodev_of_7o
+     v7e_ac=nodev_ac_of_7e v7o_ac=nodev_ac_of_7o
+     v11e=nodev_of_11e v11o=nodev_of_11o
+     v11e_ac=nodev_ac_of_11e v11o_ac=nodev_ac_of_11o

* Definition of the output variables.

end_circuit

```

2. Solve Block 1:

```

begin_solve
  solve_type=startup
  initial_sol initialize
  method: t_startup=0

* Do a "start-up" solution. As the initial guess for the
* Newton-Raphson iterations, use the "initialize" option.
* Since we have not generated any solution prior to this,
* the "initialize" option has to be used.

end_solve

```

3. Solve Block 2:

```
begin_solve
  solve_type=trns
  initial_sol previous

* Perform a transient simulation, using the previous solution
* (obtained in the last solve block) as the initial guess for
* the Newton-Raphson iterations. Note that "initial_sol" is
* relevant only to get the transient simulation started (i.e.,
* the very first time step). For subsequent time steps, the
* solution obtained for the previous time step is always used
* as the initial guess for the N-R iterations.

begin_output
  filename=bu2.dat limit_lines=20000000
  variables: v11e
end_output

* Specify which output files are to be generated and which
* output variables are to be written to each of the files.
* Note that we write here only analog variables of interest (v11e).
* If we want to store digital variables, we should ask for one more file.
* The two types of variables cannot be written to a single file.
*
* Note that limit_lines has been specified in the above files
* since the default value (10,000) is too small. The number
* of lines which get written to the output files is larger
* than this default value, and this would cause the program
* to stop before the specified end time is reached.

method: norm_2=1.0e-5 itmax_trns=10000000 back_euler=yes
+   t_start=0 t_end=7m delt_const=1u delt_min=50n

* Specify the RHS norm ("tolerance"). The default value of
* norm_2 is 1.0e-10. However, that turns out to be too rigid
* for this problem and hence the need to change it.

* Use the backward Euler method with a constant time step of
* 1 usec.

* Specify the starting and ending times, and time step.
* Note that itmax_trns has been specified since the default
* value (10,000) is too small; the number of time points required
* for this simulation is larger than the default itmax_trns.

end_solve
```

4. Solve Block 3:

```
begin_solve
  solve_type=ac
  vary_freq from 1 to 10k type=linear n_points=200

* Above two statements perform AC analysis. The complete frequency range of
```

* interest is divided in two parts. The first range is evaluated here with
* frequency points chosen in logarithmic fashion with number of points 200.

```
begin_output
  filename=bum1.dat
  variables:
+   mag_of_vlle_ac phase_of_vlle_ac
+   mag_of_vllo_ac phase_of_vllo_ac
end_output
```

* Specify the output file and variables to be written.

end_solve

5. Solve Block 4:

```
begin_solve
  solve_type=ac
  vary_freq from 10k to 20k type=linear n_points=200
```

* Above two statements perform AC analysis for second range of frequency
* with number of points 200.

```
begin_output
  filename=bum1.dat append=yes
  variables:
+   mag_of_vlle_ac phase_of_vlle_ac
+   mag_of_vllo_ac phase_of_vllo_ac
end_output
```

* Specify the same output file and variables to be written, which are mentioned
* for first frequency range (Solve Block 3). Indicate "Append" to add the data.

end_solve

end_cf

Results:

In this example, simulated transient and frequency domain response are shown in
Figs. 3 and 4 respectively.

References:

- [1]K. R. Laker, "Equivalent circuits for the analysis and synthesis of switched-capacitor networks," Bell Syst. Tech. J., vol. 58, pp. 727-767, Mar. 1979.
- [2]Opal and J. Vlach, "Analysis and sensitivity of periodically switched linear networks," IEEE Trans. Circuits and Syst., Vol. 36, No. 4, pp. 522-532, April -1989.

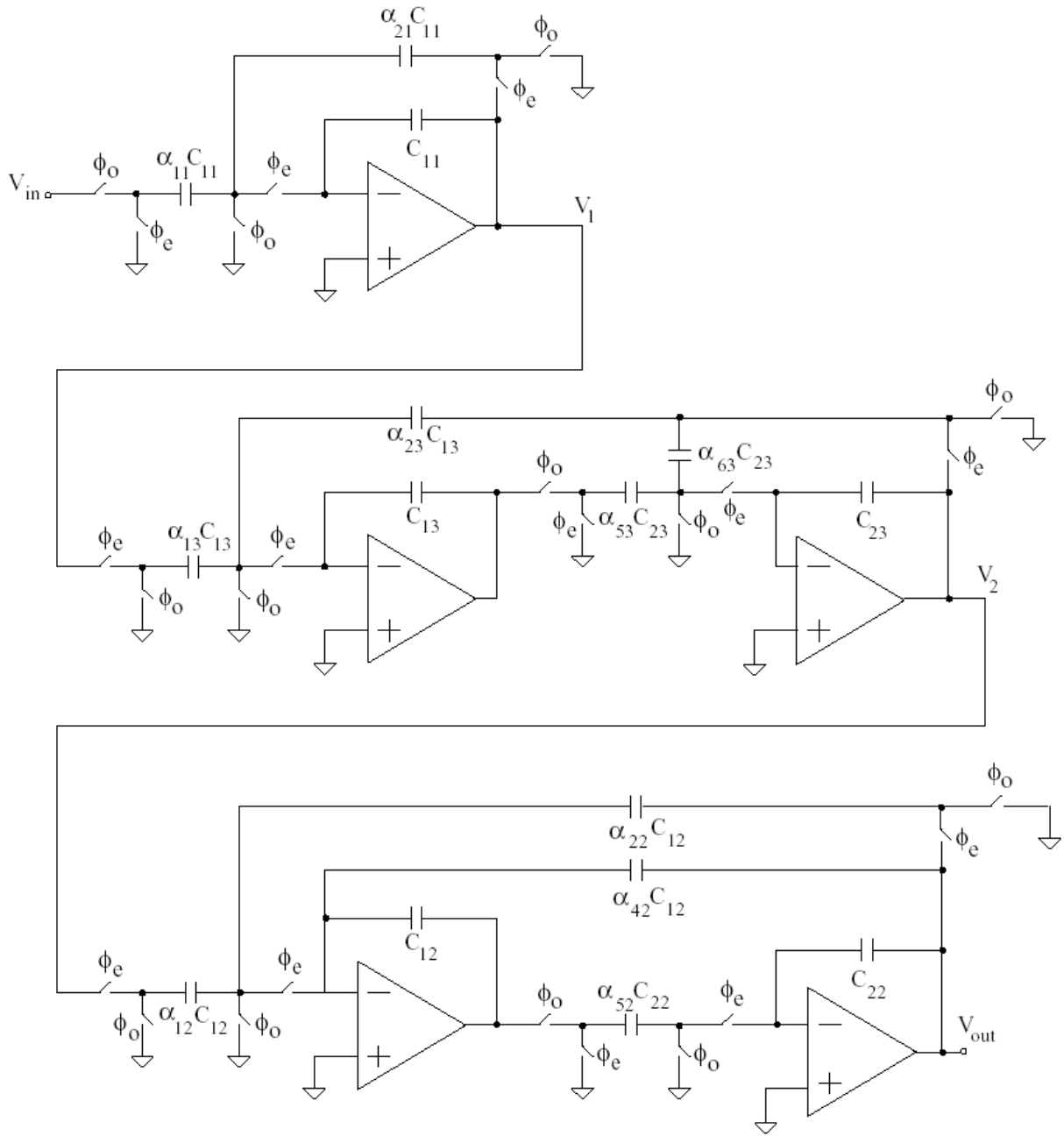


Fig. 1. Fifth-order Chebyshev Low-pass filter using cascaded approach; the circuit parameters are $\alpha_{11} = \alpha_{21} = 0.0909$, $\alpha_{13} = \alpha_{23} = \alpha_{53} = 0.2058$, $\alpha_{63} = 0.1472$, $\alpha_{12} = \alpha_{22} = \alpha_{52} = 0.3123$, $\alpha_{42} = 0.18$, $C_{11} = C_{12} = C_{22} = C_{13} = C_{23} = 1.0$ pF, $f_c = 20$ kHz.

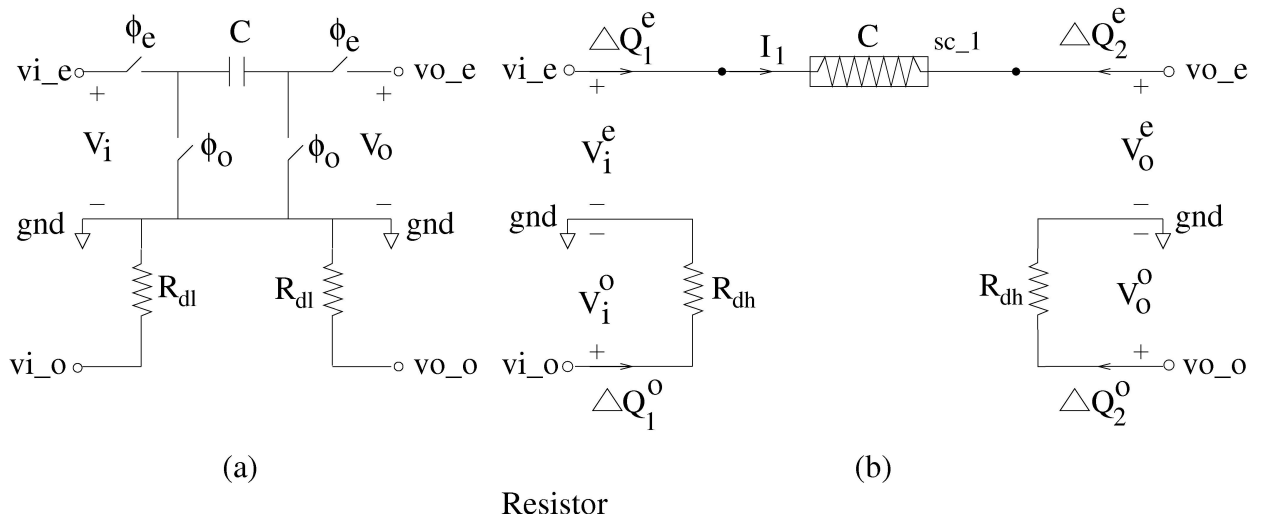


Fig. 2. Switched resistor block, Time-domain (Left) and Frequency-domain (Right).

 


Fig. 3. Transient response showing output signal at node v_{lle} for an input with frequency 600 Hz.

 


Fig. 4. Frequency-domain response plotted after output voltage converted into Gain. V1 and V2 are output of first and second stages, respectively. In circuit file, Vout is the node v11.