

schmitt\_osc\_741.sqproj

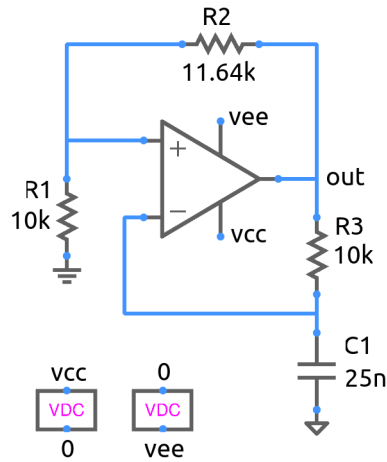


Figure 1: Oscillator circuit using a Schmitt trigger.

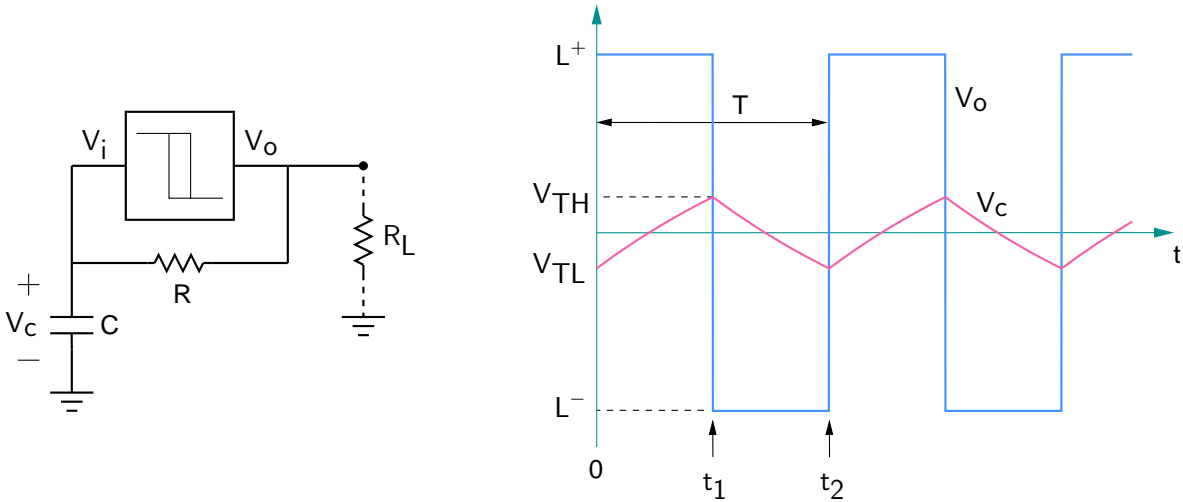


Figure 2: Waveforms for output voltage (blue) and capacitor voltage (red).

Shown in Fig. 1 is an oscillator circuit using an inverting Schmitt trigger. Fig. 2 shows the associated waveforms. The capacitor voltage  $V_C$  varies between  $V_{TL}$  and  $V_{TH}$ , the low and high thresholds of the Schmitt trigger, respectively. When  $V_o$  is high (denoted by  $L^+$  in Fig. 2), the capacitor charges toward  $L^+$ . However, when it crosses  $V_{TH}$ , the output changes to  $L^-$ . Now the capacitor starts discharging toward  $L^-$ . When it crosses  $V_{TL}$ , the output changes again, and this cycle continues.

## Exercise Set

1. Assuming  $L^+ = -L^- = L$ , show that  $V_{TL} = -V_{TH} \equiv V_T$ . Calculate  $V_T$  for  $L = 13.4\text{ V}$ .
2. Show that the period of oscillation is given by

$$T = 2RC \ln \frac{L + V_T}{L - V_T}. \quad (1)$$

3. Run the simulation, and plot  $V_o(t)$  and  $V_C(t)$ . Calculate  $T$  and compare it with the simulation result.
4. Compare the waveforms with those obtained with the LF411 Op amp model (see `schmitt_osc_411.sqproj`). Comment on the difference you observe in the waveforms.

## References

1. S. Franco, *Design with Operation Amplifiers and Analog Integrated Circuits*, McGraw-Hill, 1998.
2. A. S. Sedra, K. C. Smith, and A. N. Chandorkar, *Microelectronic Circuits: Theory and Applications*, Fifth edition, Oxford University Press, 2009.
3. J. Millman and A. Grabel, *Microelectronics*, McGraw-Hill, 1988.