
test_filter_order2.sqproj

flag_asymptote = 0

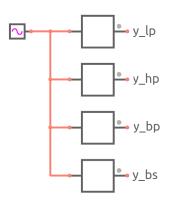

Note: Use trapezoidal method.

Exercise Set

- 1. Shown in the figure are second-order filters. Look at their parameters and check that the simulated frequency response corresponds to the specified parameter values.
- 2. Change some of the parameter values and observe the effect on the frequency response.
- 3. Simulate in time domain and verify that the filters exhibit the expected behaviour.