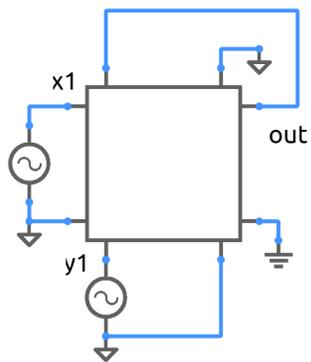


test_multiplier1.sqproj



Multiplication of two signals

Shown in the figure is a circuit to multiply two signals using an analog multiplier (implemented with an ideal behavioral model).

Exercise Set

1. Run the simulation and plot the node voltages at **x1** and **y1** versus time. Go through the help file for `multiplier_1.gme`, and with the connections shown in the figure, obtain an expression for the output voltage.
2. Compare your expression with simulation results.