

### DC–AC Converter (PE\_1ph\_VSI\_2.sqproj)

**Question:** A single-phase half–bridge voltage source inverter (VSI) shown in Fig. 1 drives an  $RL$  series load with  $R = 3\ \Omega$  and  $L = 5\ \text{mH}$ . The input dc voltage  $V_{dc} = 100\ \text{V}$  and the desired fundamental frequency is 50 Hz. Determine

- (i) % THD of the output voltage waveform.
- (ii) RMS output current at fundamental frequency

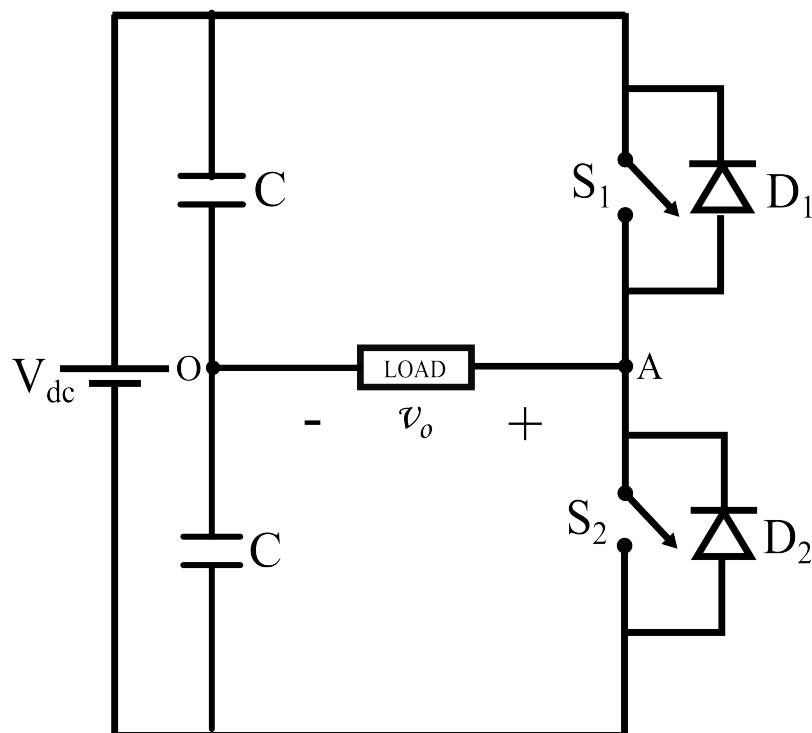


Figure 1: Half–bridge inverter

**Solution :**

For an unmodulated voltage source inverter, the  $v_o$  waveform is half wave symmetrical square, irrespective of the type of load. Therefore, the pattern of conduction of switches and diodes should be as follows.

	$v_o$	$i_o$
$S_1$	+	+
$D_1$	+	-
$S_2$	-	-
$D_2$	-	+

Assume that the inductor has some stored energy initially.

**Operation :** When the diode  $D_1$  is ON ( $0 < t < t_1$ ) and when the switch  $S_1$  is ON ( $t_1 < t < \frac{T}{2}$ ), the output voltage is positive. The inductor is storing energy from  $0 < t < \frac{T}{2}$ . Similarly, when the diode  $D_2$  is ON ( $\frac{T}{2} < t < t_2$ ) and when the switch  $S_2$  is ON ( $t_2 < t < T$ ), the output voltage is negative. The inductor is releasing energy from  $\frac{T}{2} < t < T$ .

(i)  $v_o$  waveform as shown in Fig. 2 (a).

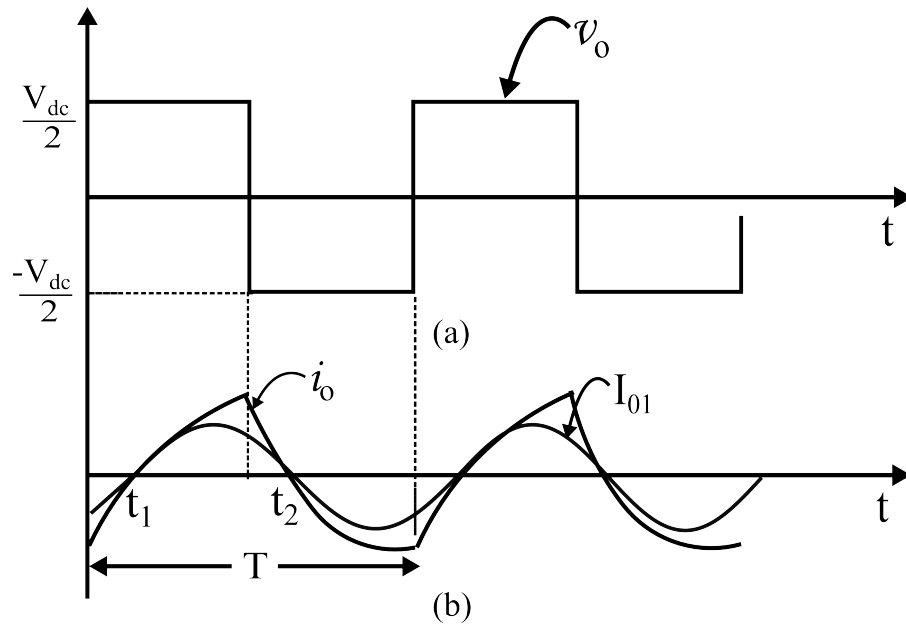


Figure 2: Output voltage and current waveforms

The waveform has half wave symmetry. Hence the Fourier series consists of odd harmonic terms alone. Also, the waveform is an odd periodic signal, i.e., only the

sine terms of the Fourier series exist.

Therefore, the trigonometric Fourier series representation of the waveform is given by the eqn. 1.

$$v_o(\omega t) = \sum_{n=1,3,5,\dots}^{\infty} \frac{4}{n\pi} \frac{V_{dc}}{2} \sin(n\omega t) \quad (1)$$

The RMS output voltage at the fundamental frequency ( $V_{01}$ ) =  $\frac{4}{\sqrt{2}\pi} \times \frac{100}{2} = 45 \text{ V}$

For a square waveform, the RMS value and the magnitude of waveform are equal.

$$\therefore V_o^{\text{rms}} = V_{dc} = 50 \text{ V}$$

The total harmonic distortion (THD) is a measurement of the harmonic distortion present in a signal and is given by

$$\% \text{THD} = \sqrt{\frac{(V_o^{\text{rms}})^2 - V_{01}^2}{V_{01}^2}} = 48.43\%$$

**NB :** % THD of a square waveform is always 48.43% irrespective of magnitude.

- (ii) The load current waveform ( $i_o$ ) is shown in Fig. 2 (b). The desired fundamental frequency is 50 Hz and therefore the fundamental load impedance ( $Z_{L1}$ ) is given by

$$Z_{L1} = \sqrt{R_1^2 + (2\pi f_1 L)^2} = 3.386 \Omega$$

The fundamental load current ( $I_{01}$ ) component is given by

$$\begin{aligned} I_{01} &= \frac{\left(4 \cdot \frac{V_{dc}}{2\pi}\right) \sin(\omega_1 t - \Phi_1)}{Z_{L1}} \quad , \quad \text{where} \quad \Phi_1 = \tan^{-1} \left( \frac{X_{L1}}{R} \right) \\ &= \frac{\frac{400}{2\pi} \sin(\omega_1 t - \Phi_1)}{3.386} \end{aligned}$$

$\therefore$  The fundamental RMS output current is given by

$$I_{01}^{\text{rms}} = \frac{400}{2\sqrt{2}\pi \times 3.386} = 13.29 \text{ A}$$

### SequelApp Exercises:

- (1) In a half-bridge VSI, with series  $RL$  load, if  $R = 2 \Omega$ , find the value of inductor such that fundamental RMS output current is 20 A. The desired fundamental frequency is 50 Hz. (Take  $V_{dc} = 120 \text{ V}$ )

Verify your answer using SequelApp.