

AC voltage controller - 1 (PE_AC_Controller_1.sqproj)

Question: For the single phase AC voltage controller shown in Fig. 1,

- Find the minimum firing angle (α) which will enable control of power flow into the load.
- For the above firing angle, find the power transferred to the load and the source power factor.

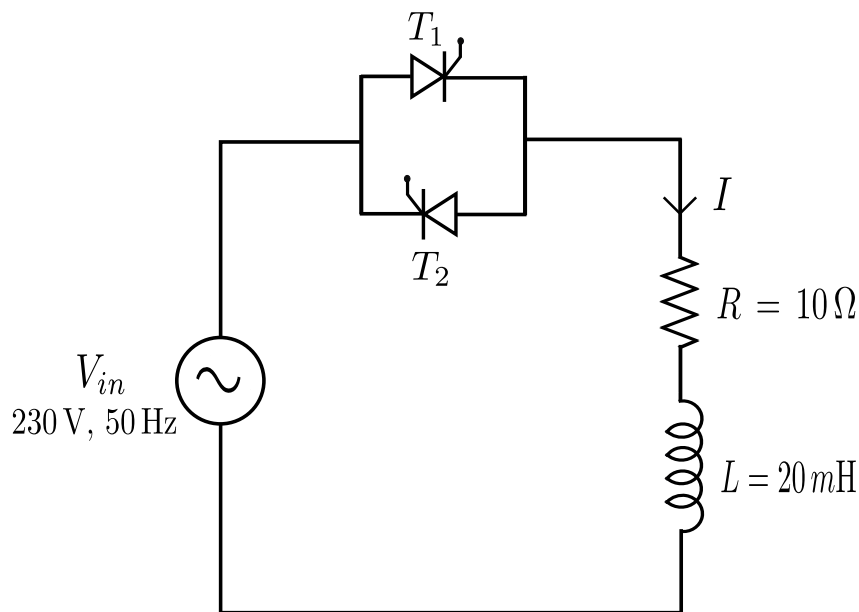


Figure 1: Single phase AC voltage controller

Solution:

- For the circuit shown in Fig. 1, the thyristor T_1 is forward biased during $\omega t = 0$ to π . The firing angle α should be in this interval. At $\omega t = \pi$ the source and load voltages are zero, but load current is non-zero due to the presence of inductance. The current still flows through thyristor T_1 until the extinction angle β . Thyristor T_2 cannot be fired until β since it is reverse biased by voltage drop in T_1 .

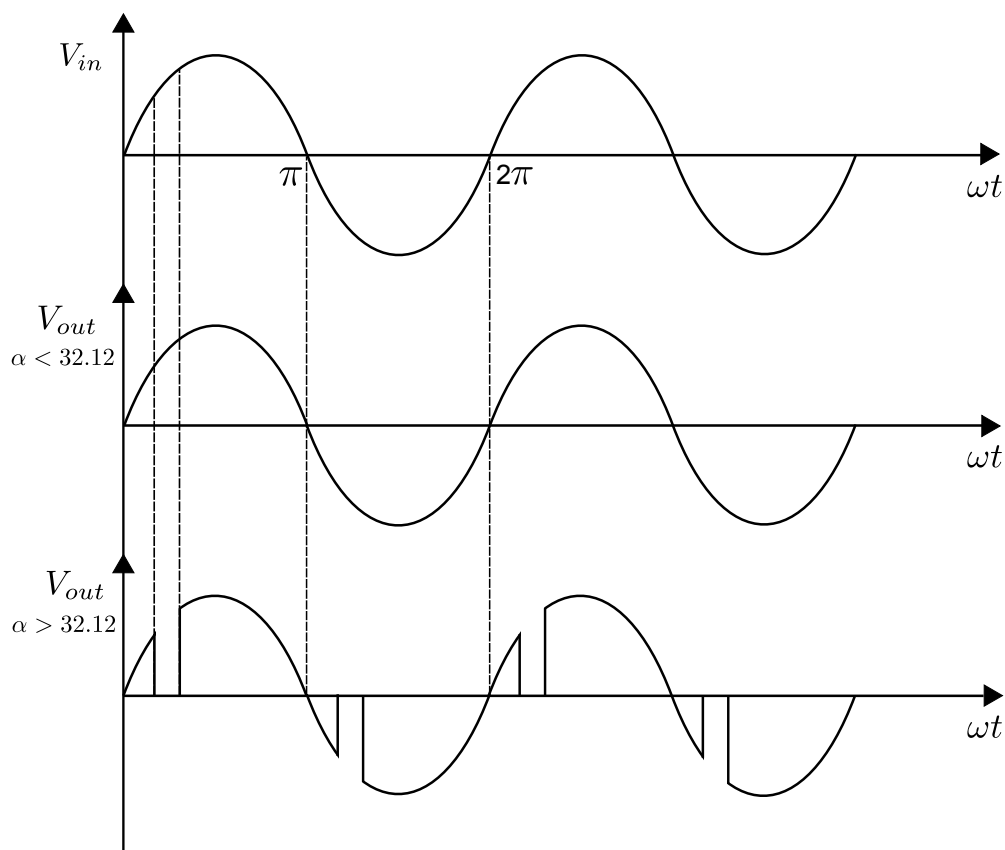


Figure 2: Output waveforms of single phase AC voltage controller

Solving KVL for the circuit.

For $\alpha < \omega t < \beta$,

$$V_{out} = V_m \sin(\omega t) = RI + L \frac{dI}{dt} \quad (1)$$

The solution of this equation,

$$I = \frac{V_m}{Z} \sin(\omega t - \phi) + Ae^{(-R/L)t} \quad (2)$$

where,

$$Z = \sqrt{(R^2 + \omega L^2)} \quad (3)$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) \quad (4)$$

The current flows through thyristor for ϕ duration after the source voltage reverses its polarity. So this is the minimum firing angle α of the circuit. The minimum firing angle required for controlling the power flow to load,

$$\alpha = \tan^{-1} \left(\frac{\omega L}{R} \right) = 32.12^\circ \quad (5)$$

(b) The current through the load for $\alpha = 32.12$,

$$I_{rms} = \frac{V_{in}}{Z} = \frac{230}{11.8} = 19.5 \text{ A} \quad (6)$$

The power transferred to the load for $\alpha = 32.12$,

$$P = I_{rms}^2 R = 3.8 \text{ kW} \quad (7)$$

As thyristors are considered as ideal and lossless, input power is equal to output power.

$$V_{in} I_{rms} \cos \phi = I_{rms}^2 R \quad (8)$$

The power factor for $\alpha = 32.12$,

$$\cos \phi = \frac{I_{rms}^2 R}{I_{rms} V_{in}} = 0.847 \quad (9)$$

SequelApp Exercises:

For the circuit in Fig. 1, find the following.

- (a) The value of R required to enable control power flow into the load at a firing angle $\alpha = 20^\circ$.
- (b) For the above firing angle, find the power transferred to the load and the source power factor.

Verify your answers using SequelApp.