

Fully Controlled Rectifier - 2 (PE_rectifier_3.sqproj)

Question: For the fully controlled rectifier circuit shown in Fig. 1,

- Find the minimum value of firing angle (α) required to turn on the thyristors.
- For $\alpha=45^\circ$, find the average output voltage (V_{out}), average output current (I_{out}), and power (P) delivered to the battery E .

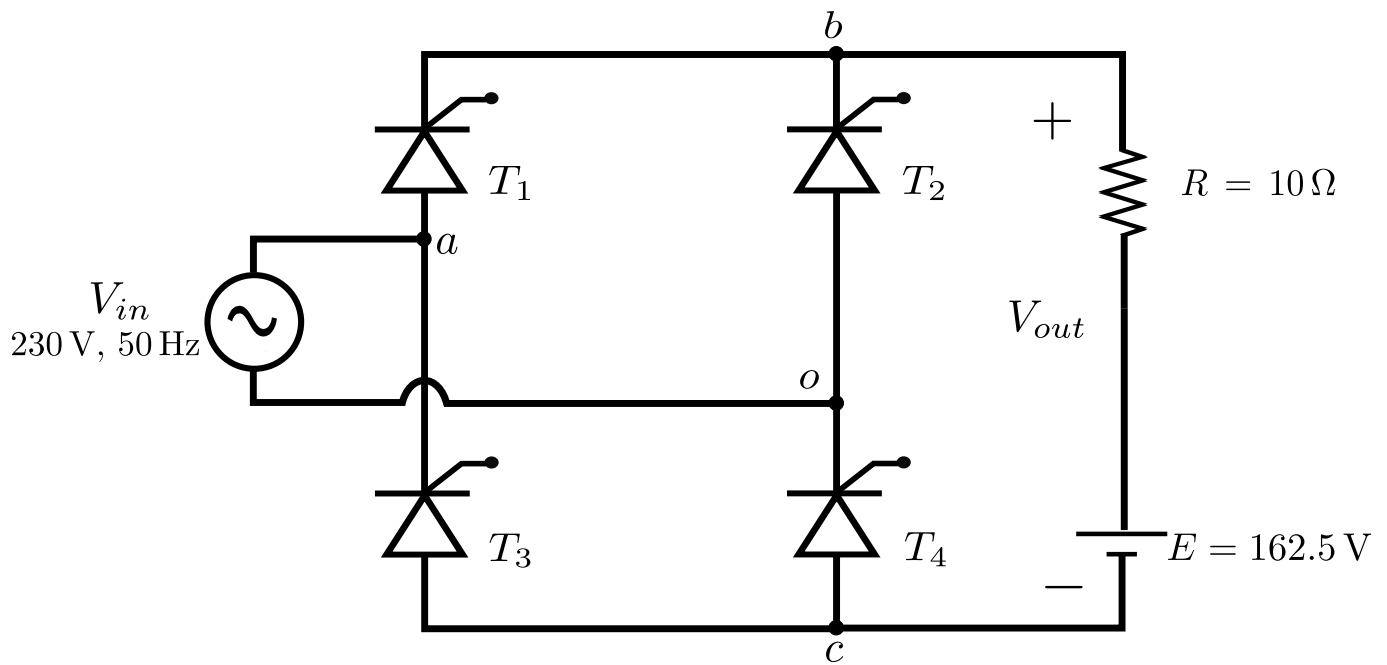


Figure 1: Fully controlled rectifier with RE load.

Solution:

- Let us assume the minimum firing angle as θ . We know that thyristor should be fired when the voltage across it is positive.

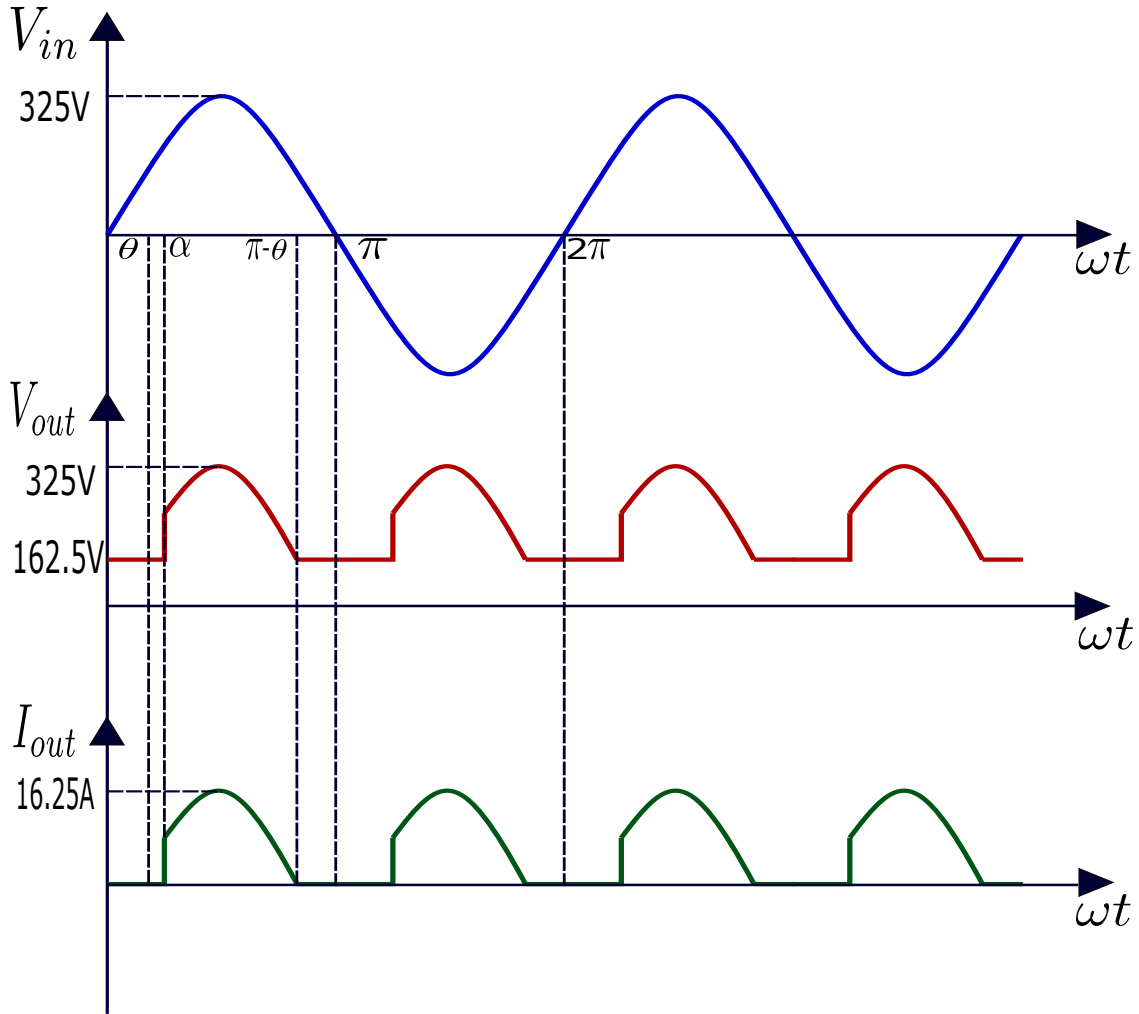


Figure 2: Plots of V_{in} , V_{out} and I_{out} vs ωt

In positive half cycle, voltage across thyristors T_1 and T_4 is negative when V_{in} is less than E and is positive when V_{in} is greater than E . Minimum firing angle, θ is the angle at which V_{in} is equal to E .

$$V_m \sin \theta = E \quad (1)$$

$$\alpha = \sin^{-1} \left(\frac{E}{V_m} \right) \quad (2)$$

$$\theta = \sin^{-1} \left(\frac{162.5}{325} \right) = 30^\circ \quad (3)$$

(b) As shown in Fig. 2, the current starts flowing through load when thyristors are fired. i.e. from $\alpha = 45^\circ$ and as it is RE load the thyristor turns off at 150° (the angle after which voltage across the thyristor is negative). So the load current is zero from 150° to 180° . By KVL, the output voltage is identical to input voltage when the current flows through load and it is equal to E when current does not flow. So, the average output voltage,

$$V_{out} = \frac{1}{\pi} \left(\int_0^{\pi/4} E.d\omega t + \int_{\pi/4}^{5\pi/6} V_m \sin \omega t.d\omega t + \int_{5\pi/6}^{\pi} E.d\omega t \right) \quad (4)$$

$$V_{out} = \frac{1}{\pi} (V_m(\cos \alpha + \cos \theta) + E(\alpha + \theta)) \quad (5)$$

$$V_{out} = \frac{1}{\pi} \left(325 \left(\cos \frac{\pi}{4} + \cos \frac{\pi}{6} \right) + 162.5 \left(\frac{\pi}{4} + \frac{\pi}{6} \right) \right) = 230V \quad (6)$$

From Fig 2, the average current through load

$$I_{out} = \frac{1}{\pi R} \int_{\pi/4}^{5\pi/6} (V_m \sin \omega t - E) d\omega t \quad (7)$$

$$I_{out} = \frac{1}{10\pi} \left(V_m \left(\cos \left(\frac{\pi}{4} \right) - \cos \left(\frac{5\pi}{6} \right) \right) - E \left(\frac{5\pi}{6} - \frac{\pi}{4} \right) \right) = 6.75A \quad (8)$$

The power delivered to DC source E ,

$$P = E \times I_{out} = 1.09KW \quad (9)$$

SequelApp Exercises:

For the circuit shown in Fig. 1, Find the Average output voltage (V_{out}) and power delivered (P) to DC source for the following cases other circuit parameters same as in figure.

- (a) The firing angle $\alpha = 60$.
- (b) $E = 200V$ and firing angle $\alpha = 60$.

Verify your answers using SequelApp.