## Single Phase Semi-Controlled Rectifier - 1 (PE\_rectifier\_8.sqproj)

Question: For the single phase semi-controlled rectifier circuit shown in Fig. 1,

- (a) Find the average output voltage  $(V_{out})$  for the firing angle  $\alpha = 30^{\circ}$ .
- (b) Find the RMS value of the source current.

(Assume that the inductance is large enough to give a constant load current in steady state.)



Figure 1: Semi-Controlled rectifier with RL load.

## Solution:

(a) For a 1-phase semi-controlled rectifier shown in Fig. 1, the thyristor  $T_1$  is fired at  $\alpha = 30$ . From  $\alpha$  to  $\pi$  thyristor  $T_1$  and diode  $D_2$  conduct. By solving KVL, output

voltage is equal to input voltage in this duration. At  $\omega t = \pi$  input voltage  $V_{in}$  reverses its polarity and since current is continuous in the load, the current freewheels through  $T_1$  and  $D_1$  until thyristor  $T_2$  is fired. The output voltage  $V_{out}$  is zero in this duration.



Figure 2: Input and Output waveforms of single phase semi controlled rectifier

In the negative half cycle, the thyristor  $T_2$  is fired at  $\pi + \alpha$ . From  $\pi + \alpha$  to  $2\pi$  thyristor  $T_2$  and diode  $D_1$  conduct. By solving KVL, output voltage is equal to  $-V_{in}$  in this duration. At  $\omega t = 2\pi$  input voltage  $V_{in}$  reverses its polarity and since current is continuous in the load, the current freewheels through  $T_2$  and  $D_2$  until thyristor  $T_1$  is fired in the next cycle. The output voltage  $V_{out}$  is zero in this duration. The output

voltage waveform is shown in Fig. 2.

From the waveforms, the average value of output voltage,

$$V_{out} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d(\omega t) = \frac{V_m}{\pi} (1 + \cos \alpha)$$
(1)

$$V_{out} = \frac{230\sqrt{2}}{\pi} \left(1 + \frac{\sqrt{3}}{2}\right) = 193 \,\mathrm{V}$$
(2)

(b) The average load current,

$$I_{out} = \frac{V_{out}}{R} = 19.3 A \tag{3}$$

Given that the current flowing through the load is constant. From  $\alpha$  to  $\pi$  in a half cycle, the current to the load is flowing from the source. From  $\pi$  to  $\pi + \alpha$ , the current freewheels through the zero resistance path. This is shown in Fig. 2. The RMS value of the source current,

$$I_{sr} = 19.3 \times \sqrt{\frac{150}{180}} = 17.6 \,\mathrm{A}$$
 (4)

## SequelApp Exercises:

For the circuit in Fig. 1, find the following:

- (a) The firing angle ( $\alpha$ ) to get an average output voltage  $V_{out} = 150$  V.
- (b) The RMS value of the source current  $(I_{sr})$  in this case.

Verify your answers using SequelApp.