

Logic gates (DGTL\_gates\_1.sqproj)

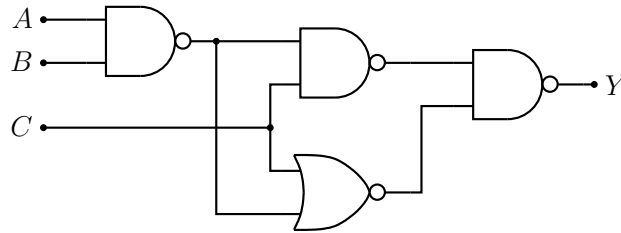


Figure 1: Logic circuit example.

**Question:** For the circuit shown in Fig. 1, find a logical expression for  $Y$ , and construct its truth table.

**Solution:**

We have  $X_2 = \overline{X_1 C}$ ,  $X_3 = \overline{X_1 + C}$  (see Fig. 2).

$\rightarrow Y = \overline{X_2 X_3} = \overline{\overline{X_1 C} \cdot \overline{X_1 + C}} = X_1 C + (X_1 + C)$ , using De Morgan's theorem.

Using the identity  $A + AB = A$ , we get

$$Y = (X_1 + X_1 C) + (C + X_1 C) = X_1 + C = \overline{A B} + C = \overline{A} + \overline{B} + C.$$

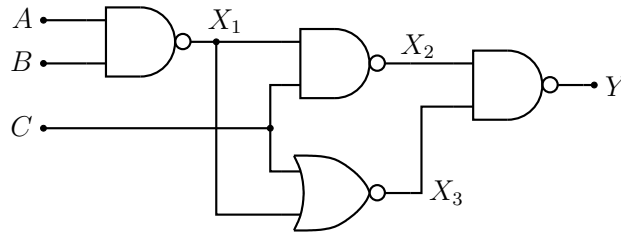


Figure 2: Logic circuit of Fig. 1, redrawn with additional variables shown.

From the above expression, we can construct the truth table for  $Y$  as given below.

$A$	$B$	$C$	$Y$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

**SequelApp Exercises:** For the circuit shown in Fig. 3, find a logical expression for  $Y$ , and construct its truth table.

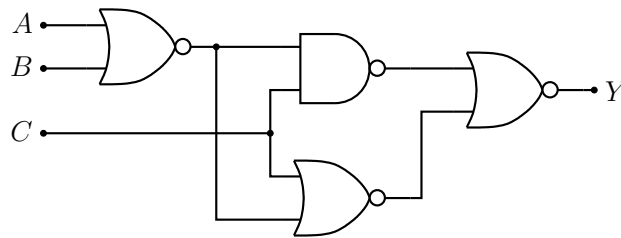


Figure 3: Logic circuit example.

Verify your answers using SequelApp.