

Oscillator using 555 timer (EC_555_1.sqproj)

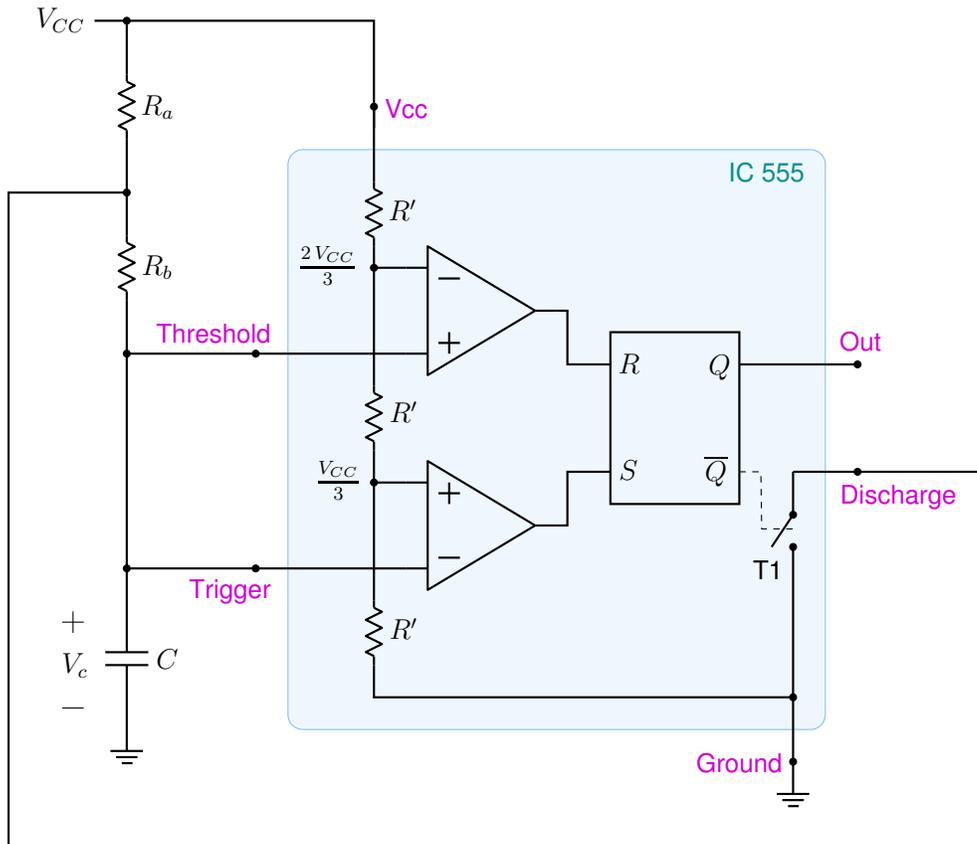


Figure 1: Oscillator circuit based on the 555 timer.

Question: For the oscillator circuit shown in Fig. 1, $R_a = 0.5\text{ k}$, $R_b = 0.5\text{ k}$, and $C = 0.5\ \mu\text{F}$.

- (a) Draw the waveforms $V_{\text{out}}(t)$ and $V_c(t)$.
- (b) Find the oscillation frequency and the duty cycle.

Solution:

The trigger and threshold inputs are tied together in this circuit, and we have $V_{\text{trigger}} = V_{\text{threshold}} = V_c$. The circuit operation can be understood by realizing that the following conditions hold (see Fig. 2):

$V_{CC}/3 < V_c(t) < 2V_{CC}/3$	$R = 0, S = 0$	flip-flop holds its state.
$V_c(t) < V_{CC}/3$	$R = 0, S = 1$	flip-flop is set ($Q = 1$).
$V_c(t) > 2V_{CC}/3$	$R = 1, S = 0$	flip-flop is reset ($Q = 0$).

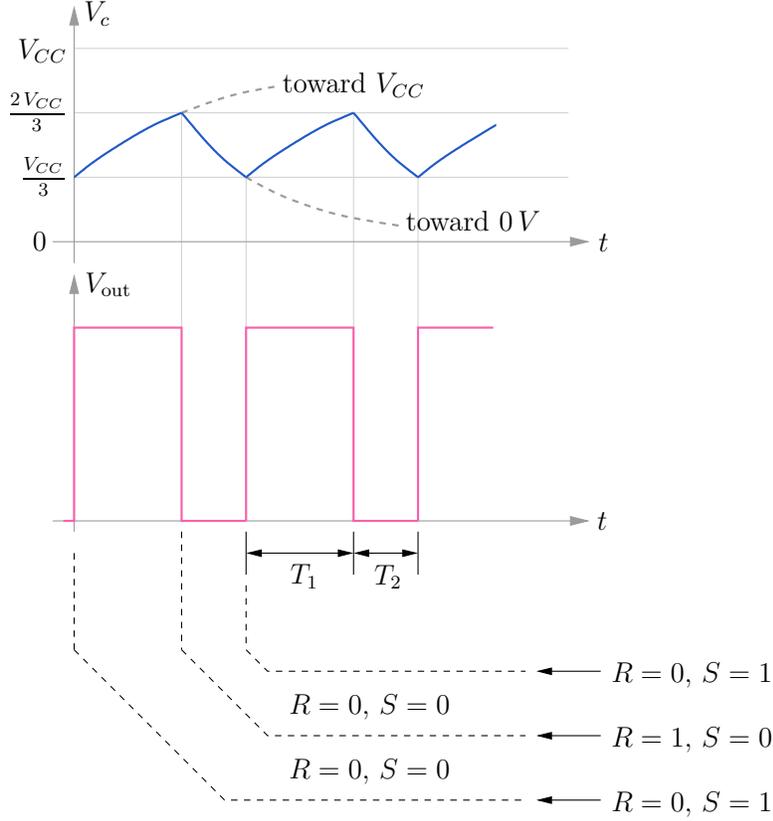


Figure 2: Waveforms for the oscillator circuit of Fig. 1.

Consider the interval marked T_1 in Fig. 2. During this time, $Q = 1$, the switch T1 is open, and the capacitor charges toward V_{CC} through $(R_a + R_b)$. However, as soon as V_c reaches $2V_{CC}/3$, R becomes 1 (S is still 0), and the flip-flop gets reset to $Q = 0$.

When Q becomes 0, \bar{Q} becomes 1, and the switch T1 closes. The capacitor now starts discharging toward $0V$ through R_b . However, when V_c crosses $V_{CC}/3$, S becomes 1 (R is still 0), and the flip-flop gets set to $Q = 1$, bringing us back to the T_1 phase. The output keeps oscillating between 0 and 1, as shown in Fig. 2.

The intervals T_1 and T_2 can be computed using the above limits for $V_c(t)$ and the appropriate time constants ($\tau_1 = (R_a + R_b)C$ during the charging phase, and $\tau_2 = R_b C$ during the discharging phase). The result is,

$$T_1 = (R_a + R_b) C \ln 2, \quad (1)$$

$$T_2 = R_b C \ln 2. \quad (2)$$

The oscillation frequency is

$$f = \frac{1}{T_1 + T_2} = \frac{1}{(R_a + 2R_b)C \ln 2}, \quad (3)$$

and the duty cycle D is

$$D \equiv \frac{T_1}{T_1 + T_2} = \frac{R_a + R_b}{R_a + 2R_b}. \quad (4)$$

Substituting the given component values, we get $T = 0.52$ msec, $f = 1.92$ kHz, and $D = 0.67$, i.e., 67%.

SequelApp Exercises: Find R_a and R_b to obtain $f = 1$ kHz and $D = 75\%$, assuming C to be $0.5 \mu\text{F}$. Verify your answers using SequelApp.