

## BJT Widlar current source (mirror) (EC.bjt.widlar\_1.sqproj)

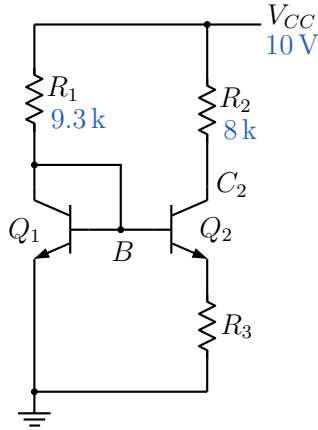


Figure 1: Widlar current source using bipolar transistors.

**Question:** Consider the Widlar current source shown in Fig. 1.

- (a) Find  $R_3$  in order to obtain  $I_{C2} = 10 \mu\text{A}$ .
- (b) For the above value of  $R_3$ , what is  $V_{C2}$ ?

**Solution:**

Assuming the BJTs to be operating in the active region, we get

$$I_{R1} \approx I_{C1} = \frac{V_{CC} - 0.7}{R_1}. \quad (1)$$

Since  $I_C \approx I_s e^{V_{BE}/V_T}$  in the active mode, we have  $V_{BE} = V_T \ln(I_C/I_s)$  for each of the transistors. Using these equations, we can write KVL for the loop involving the two B-E junctions as

$$V_{BE1} = V_{BE2} + I_{C2} R_3 \rightarrow V_T \ln(I_{C1}/I_{s1}) = V_T \ln(I_{C2}/I_{s2}) + I_{C2} R_3. \quad (2)$$

If the two transistors are identical, we have

$$V_T \ln(I_{C1}/I_{C2}) = I_{C2} R_3. \quad (3)$$

Solving this equation for  $R_3$  (with  $V_T = 0.02585 \text{ V}$ ), we obtain  $R_3 = 11.9 \text{ k}$ . The collector voltage of  $Q_2$  is

$$V_{C2} = V_{CC} - I_{C2} R_2 = 10 - 10 \mu\text{A} \times 8 \text{ k}\Omega = 9.92 \text{ V}. \quad (4)$$

**SequelApp Exercises:** For the Widlar current source of Fig. 1,

(a) Find  $R_3$  in order to obtain  $I_{C2}$  equal to (i)  $20\ \mu\text{A}$ , (ii)  $30\ \mu\text{A}$ .

(b) Find  $I_{C2}$  for  $R_3$  equal to (i)  $7.5\ \text{k}$ , (ii)  $15\ \text{k}$ .

Verify your answers using SequelApp.