

DAC with R - $2R$ ladder network (EC_dac_1.sqproj)

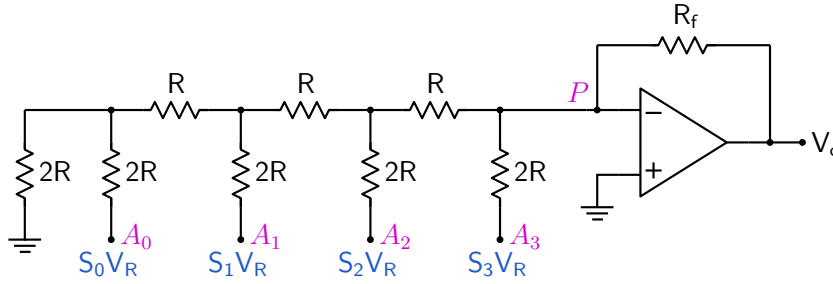


Figure 1: DAC using R - $2R$ ladder network.

Question: In the DAC circuit shown in Fig. 1, $R = R_f = 10\text{ k}$, and $V_R = 5\text{ V}$. The digital input number is represented by the variables S_3, S_2, S_1, S_0 , with S_3 as the MSB and S_0 as the LSB. The voltage at node A_k is V_R if $S_k = 1$ and 0 V otherwise. Find V_o if S_1 is 1 and S_3, S_2, S_0 are all 0.

Solution:

To obtain V_o , we will replace the R - $2R$ network with its Thevenin equivalent circuit, as shown in Fig. 2. The computation of the Thevenin resistance and Thevenin voltage is shown in Figs. 3 and 4, respectively, where repeated use of Thevenin's theorem has been made to simplify the circuit systematically.

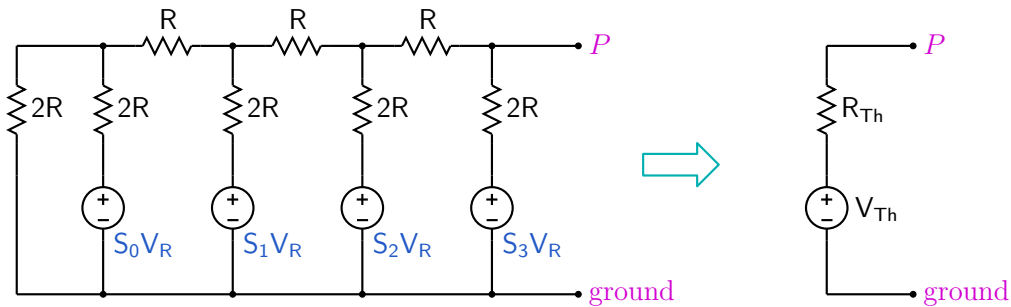


Figure 2: Representation of R - $2R$ ladder with Thevenin equivalent circuit.

Finally, we replace the R - $2R$ network in the original DAC circuit of Fig. 1 with its Thevenin equivalent circuit and obtain the circuit shown in Fig. 5. This circuit is simply an inverting amplifier, and the output voltage is given by

$$V_o = -\frac{R_f}{R} V_{Th} = -\frac{V_R}{8} = -0.625\text{ V}, \quad (1)$$

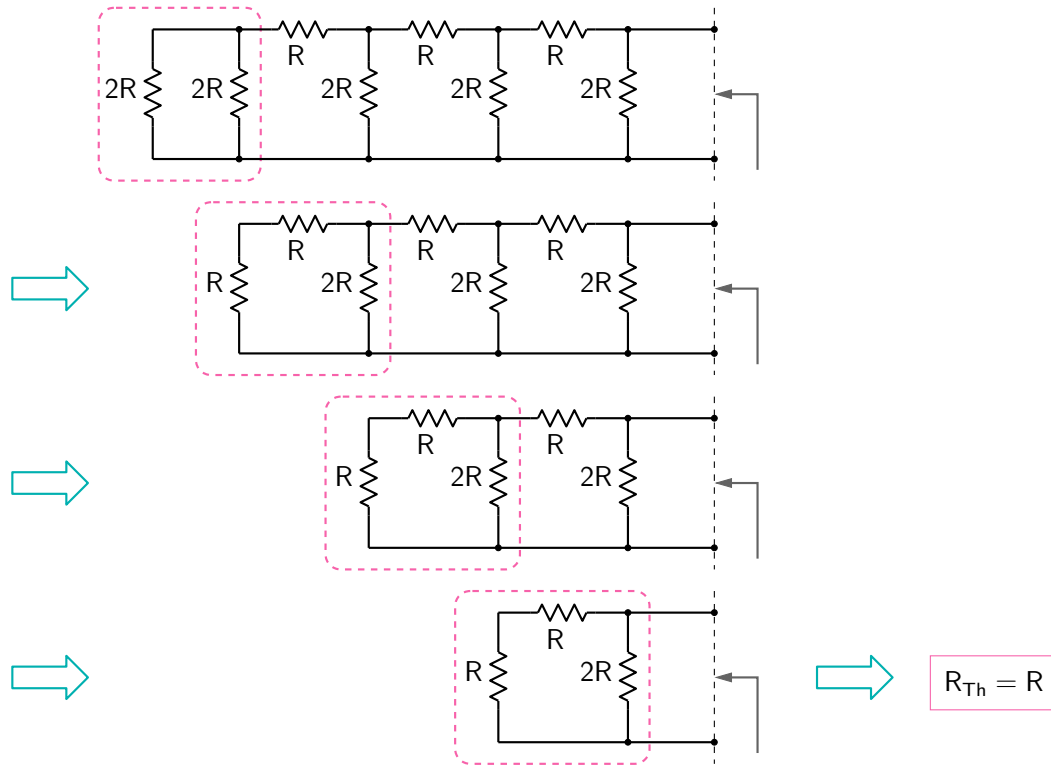


Figure 3: Thevenin resistance calculation for the R - $2R$ ladder network.

since R_f and R are equal.

SequelApp Exercises: Answer the following and verify using SequelApp.

1. Find V_o for the following input binary numbers.
 - (a) $S_3S_2S_1S_0 = 1000$.
 - (b) $S_3S_2S_1S_0 = 0100$.
 - (c) $S_3S_2S_1S_0 = 0001$.

2. Using superposition, find V_o for the following input binary numbers.
 - (a) $S_3S_2S_1S_0 = 1001$.
 - (b) $S_3S_2S_1S_0 = 1010$.

3. Find the input binary numbers ($S_3S_2S_1S_0$) which will give the following outputs.
 - (a) $V_o = -1.875$ V.
 - (b) $V_o = -1.5625$ V.

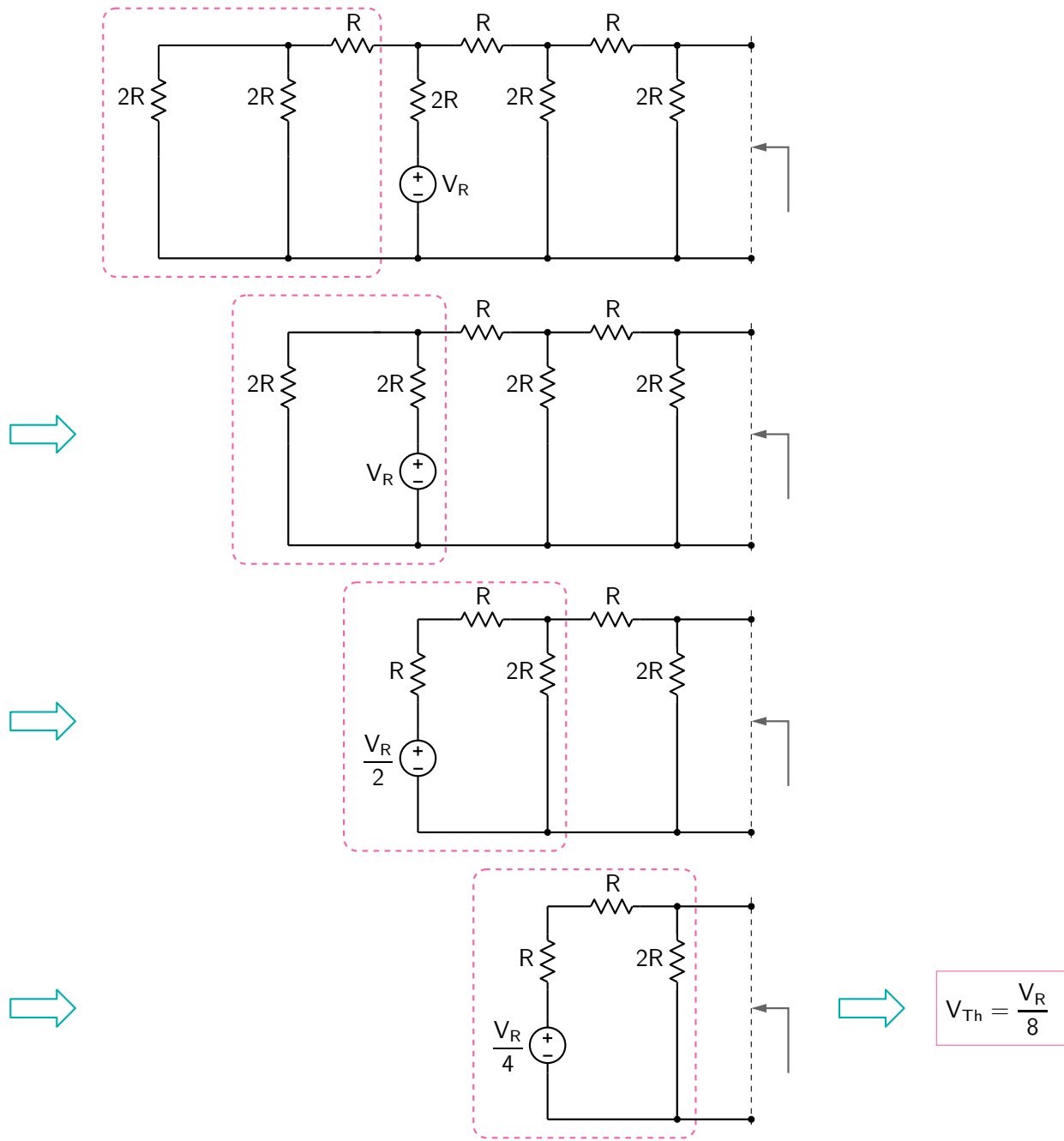


Figure 4: Thevenin voltage calculation for the $R-2R$ ladder network.

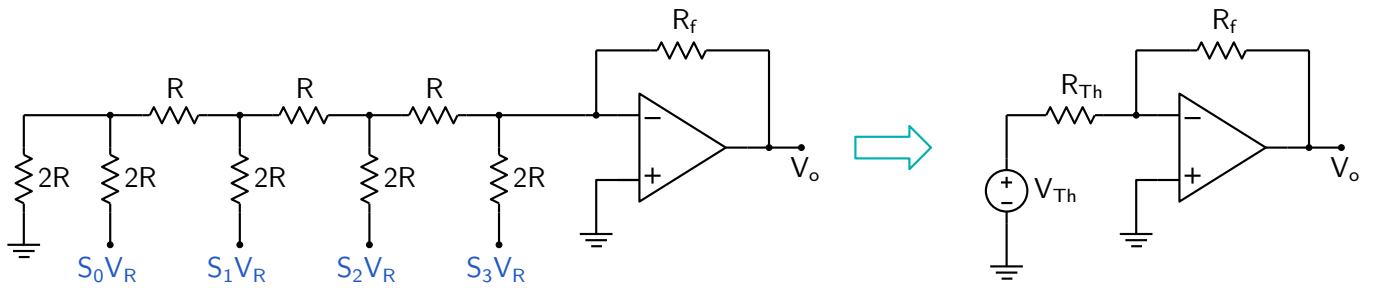


Figure 5: Original DAC circuit with $R-2R$ ladder network replaced with its Thevenin equivalent circuit.