

Half-wave rectifier (EC_diode_6.sqproj)

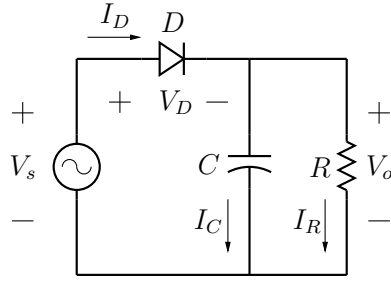


Figure 1: Half-wave rectifier.

Question: In the half-wave rectifier circuit shown in Fig. 1, the source voltage has an amplitude $V_m = 15$ V and frequency $f = 50$ Hz. Consider the diode to be ideal (i.e., $V_{on} = 0$ V). With $R = 500 \Omega$, what is the minimum value of C if the output ripple is to be limited to $V_R = 1$ V? What is the peak diode current i_D^{\max} in that case?

Solution:

Fig. 2 shows V_i , V_o , V_D , I_D , and I_C versus time. When the diode is off, the capacitor discharges through the load resistor (see the interval T_2 in the figure). The capacitor current is nearly constant and is given by

$$C \frac{dV_o}{dt} \approx C \frac{V_R}{T} = I_R^{\text{avg}} = \frac{V_m + (V_m - V_R)}{2} \times \frac{1}{R}. \quad (1)$$

Solving this equation, we get

$$C = \frac{14.5 \text{ V}}{500 \Omega} \times \frac{20 \times 10^{-3} \text{ sec}}{1 \text{ V}} = 580 \mu\text{F}. \quad (2)$$

The peak diode current can be estimated by first computing ωT_c in Fig. 2 as

$$(V_m - V_R) = V_m \cos(-\omega T_c) \rightarrow \omega T_c = \cos^{-1} \left(1 - \frac{V_R}{V_m} \right) = \cos^{-1} \left(1 - \frac{T}{RC} \right). \quad (3)$$

The peak diode current is then given by

$$\begin{aligned} I_D^{\text{peak}} &= C \frac{d}{dt} (V_m \cos \omega t) \Big|_{t=-T_c} + \frac{V_m - V_R}{R} \\ &= -\omega C V_m \sin(-\omega T_c) + \frac{14 \text{ V}}{500 \Omega} \\ &= \omega C V_m \sin \omega T_c + 0.028 \\ &= \left[(2\pi \times 50 \text{ Hz}) \times (580 \times 10^{-6} \text{ F}) \times (15 \text{ V}) \times \sin 21^\circ \right] + 0.028 \\ &= 0.98 + 0.028 \approx 1 \text{ A}. \end{aligned}$$

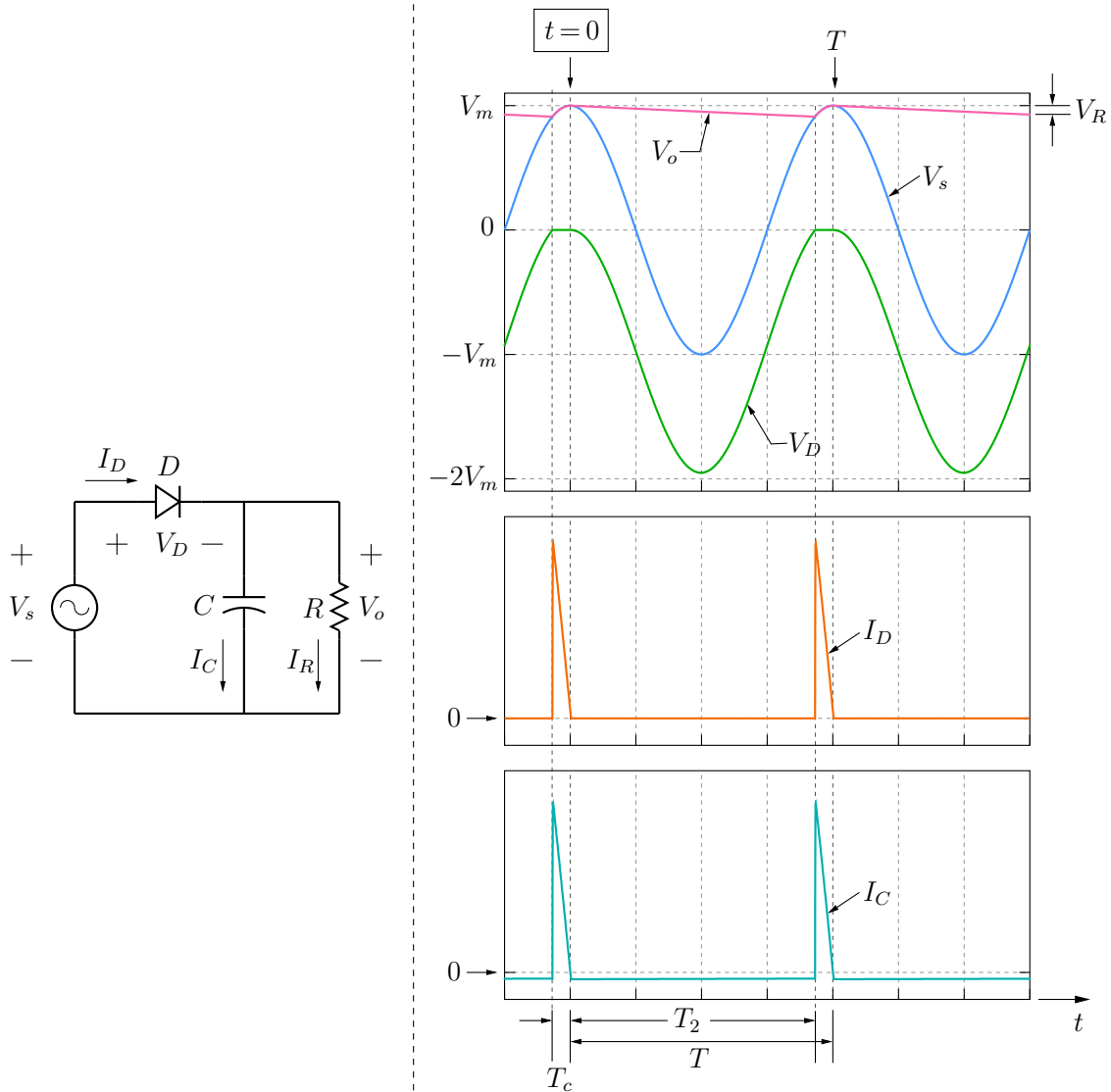


Figure 2: Voltage and current waveforms for a half-wave rectifier.

SequelApp Exercises: If R is $200\ \Omega$, what is the minimum value of C required to limit the ripple voltage V_R to $1.5\ \text{V}$? What is i_D^{\max} in that case?

Verify your answer using SequelApp.