

Mesh Analysis-1 (EC\_mesh\_1.sqproj)

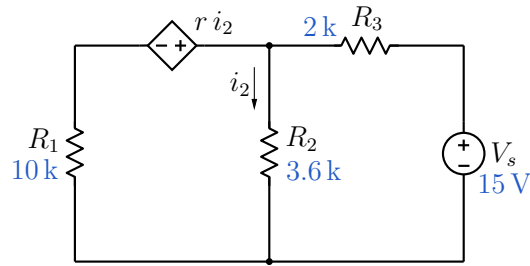


Figure 1: Mesh analysis example.

**Question:** In the circuit shown in Fig. 1, find the current  $i_2$  using mesh analysis with  $r = 1.6\text{ k}$ .

**Solution:**

To begin with, we define mesh currents, as shown in Fig. 2. In terms of the mesh currents, we can write the following KVL equations.

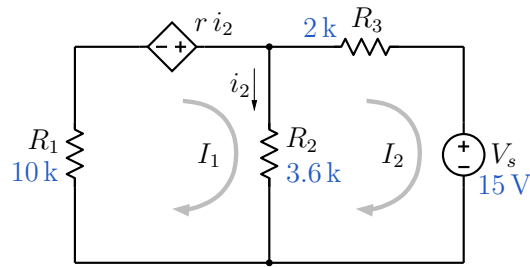


Figure 2: Circuit of Fig. 1 with mesh currents.

$$R_1 I_1 - r(I_1 - I_2) + (I_1 - I_2)R_2 = 0, \quad (1)$$

$$(I_2 - I_1)R_2 + I_2 R_3 + 15 = 0. \quad (2)$$

Collecting terms in  $I_1$  and  $I_2$ , we get

$$I_1(R_1 - r + R_2) + I_2(r - R_2) = 0, \quad (3)$$

$$I_1(-R_2) + I_2(R_2 + R_3) = -15. \quad (4)$$

With currents expressed in mA and resistances in  $\text{k}\Omega$ , we get

$$I_1(10 - 1.6 + 3.6) + I_2(1.6 - 3.6) = 0, \quad (5)$$

$$I_1(-3.6) + I_2(3.6 + 2) = -15. \quad (6)$$

After simplifying the above equations, we get

$$I_1(12) + I_2(-2) = 0, \quad (7)$$

$$I_1(-3.6) + I_2(5.6) = -15. \quad (8)$$

Solving Eqs. 7 and 8, we obtain  $I_1 = -0.5 \text{ mA}$ ,  $I_2 = -3 \text{ mA}$ . The current  $i_2$  in Fig. 1 is therefore

$$i_2 = I_1 - I_2 = 2.5 \text{ mA}. \quad (9)$$

**SequelApp Exercises:** Find  $i_2$  in the circuit of Fig. 1 for the following component values:

$R_1 = 1 \text{ k}$ ,  $R_2 = 10 \text{ k}$ ,  $R_3 = 2 \text{ k}$ ,  $r = 6 \text{ k}$ ,  $V_s = 10 \text{ V}$ .

Verify your answers using SequelApp.