

Network Theorems-2 (EC\_network\_2.sqproj)

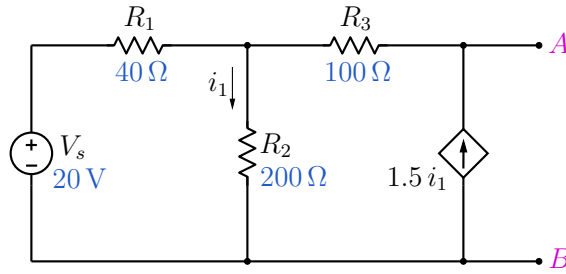


Figure 1: Thevenin theorem example.


**Question:** For the circuit shown in Fig. 1,

- (a) Find the Thevenin equivalent circuit as seen from  $AB$ .
- (b) Find the power absorbed by a resistance  $R_L = 100\ \Omega$  connected between  $A$  and  $B$ .


(Reference: “Engineering Circuit Analysis,” by W.H. Hayt and J.E. Kemmerly)

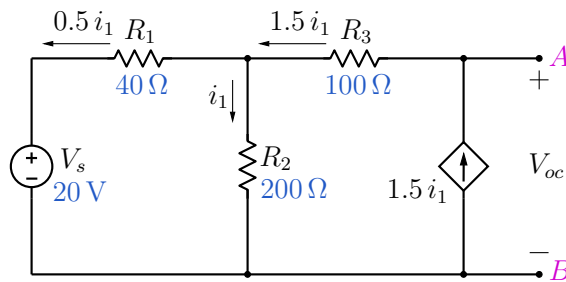**Solution:**

Let us first find  $V_{oc}$ , the open-circuit voltage between  $A$  and  $B$  (see Fig. 2 (a)). Using KCL,



(a)

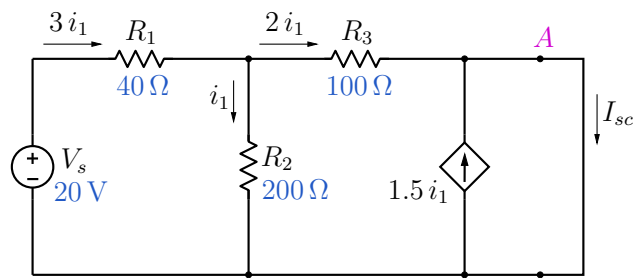

(b)

Figure 2: Calculation of (a)  $V_{oc}$ , (b)  $I_{sc}$  for the circuit of Fig. 1.

we find the current through  $R_1$  to be  $0.5 i_1$ . KVL for the loop involving  $V_s$ ,  $R_2$ , and  $R_1$  gives

$$V_s - R_2 i_1 + R_1 \times 0.5 i_1 = 0, \quad (1)$$

from which we get  $i_1 = 1/9$  A.  $V_{oc}$  can then be found as

$$V_{oc} = 1.5 i_1 R_3 + i_1 R_2 = 38.9 \text{ V}. \quad (2)$$

Next, we find the short-circuit current  $I_{sc}$  (see Fig. 2(b)). Since the voltage drops across  $R_2$  and  $R_3$  are equal, the current through  $R_3$  must be  $2 i_1$ , as shown in the figure. Using KCL, we find the current through  $R_1$  to be  $3 i_1$ . KVL gives

$$-V_s + 3 i_1 R_1 + i_1 R_2 = 0. \quad (3)$$

Solving this equation, we obtain  $i_1 = 1/16$  A. The short-circuit current can now be obtained using KCL as

$$I_{sc} = 2 i_1 + 1.5 i_1 = 3.5 i_1 = 0.219 \text{ A}. \quad (4)$$

The Thevenin equivalent circuit is therefore given by

$$V_{Th} = V_{oc} = 38.9 \text{ V}, \quad R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{38.9}{0.219} \approx 178 \Omega. \quad (5)$$

When  $R_L = 100 \Omega$  is connected (see Fig. 3), the power absorbed by it is

$$P_L = I_L^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L = 1.96 \text{ W}. \quad (6)$$

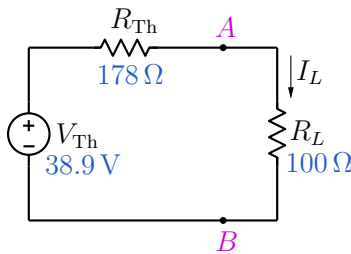


Figure 3: Thevenin equivalent circuit with  $R_L$  connected between  $A$  and  $B$ .

**SequelApp Exercises:** Find  $V_{Th}$ ,  $R_{Th}$ , and  $I_{sc}$  for each of the following cases (with other component values as shown in Fig. 1). Verify your answers using SequelApp.

1. The CCCS current is given by  $3 i_1$  (instead of  $1.5 i_1$ ).
2.  $V_s$  is changed from 20 V to 10 V.