

Network Theorems-3 (EC\_network\_3.sqproj)

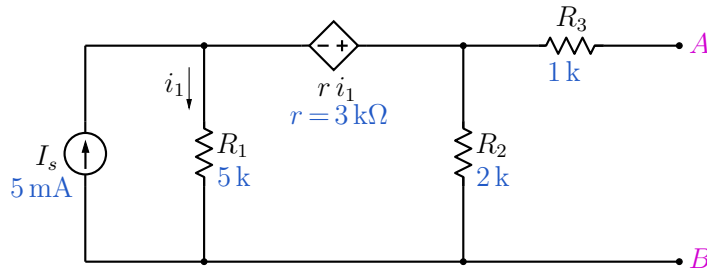


Figure 1: Thevenin theorem example.

**Question:** For the circuit shown in Fig. 1, find the Thevenin equivalent circuit as seen from  $AB$ .

**Solution:**

First, we find the open-circuit voltage  $V_{oc}$  (see Fig. 2). Using KCL, we know that the current through  $R_2$  is  $(I_s - i_1)$ . We can now write the following KVL equation.

$$-R_1 i_1 - r i_1 + (I_s - i_1) R_2 = 0. \quad (1)$$

$$\rightarrow i_1 = I_s \times \frac{R_2}{R_1 + R_2 + r} = 5 \text{ mA} \times \frac{2 \text{ k}\Omega}{8 \text{ k}\Omega} = 1 \text{ mA}. \quad (2)$$

$V_{oc}$  is the same as the drop across  $R_2$  (since the current through  $R_3$  is zero) and is given by

$$V_{oc} = (I_s - i_1) \times R_2 = (5 - 1) \text{ mA} \times 2 \text{ k}\Omega = 8 \text{ V}. \quad (3)$$

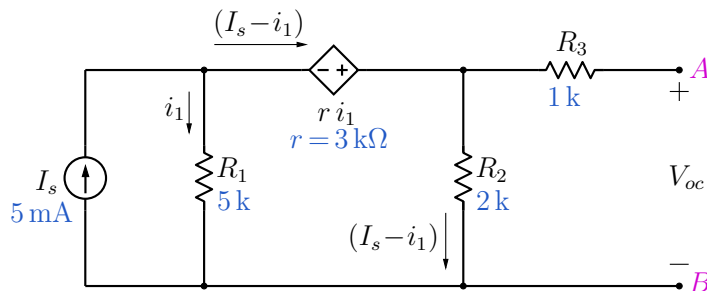


Figure 2: Calculation of  $V_{oc}$  for the circuit of Fig. 1.

Next, we find the short-circuit current  $I_{sc}$  (see Fig. 3). Since  $R_2$  and  $R_3$  have the same voltage drop, we have

$$\frac{i_{R2}}{i_{R3}} = \frac{R_3}{R_2} = \frac{1}{2} \rightarrow i_{R2} = \frac{I_{sc}}{2}, \quad (4)$$

as shown in the figure. Using KCL at nodes  $C$  and  $D$ , we get

$$i_1 = I_s - \frac{3I_{sc}}{2}. \quad (5)$$

KVL gives the following equation.

$$-i_1 R_1 - r i_1 + R_2 \frac{I_{sc}}{2} = 0. \quad (6)$$

Substituting for  $i_1$  from Eq. 5, we get

$$-\left(I_s - \frac{3}{2} I_{sc}\right) (R_1 + r) + R_2 \frac{I_{sc}}{2} = 0, \quad (7)$$

which can be solved for  $I_{sc}$  to get

$$I_{sc} = I_s \times \frac{(R_1 + r)}{\frac{3}{2}(R_1 + r) + \frac{1}{2}R_2} \approx 3.08 \text{ mA}. \quad (8)$$

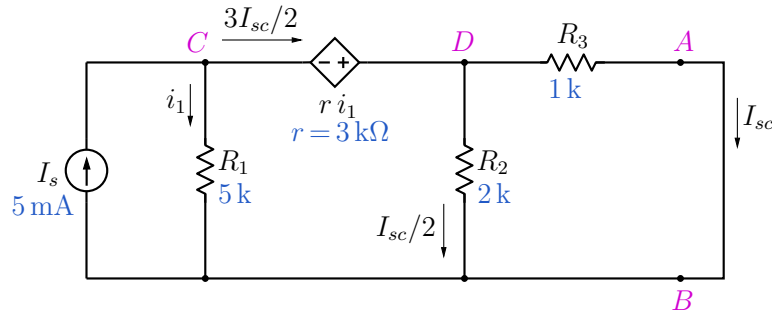


Figure 3: Calculation of  $I_{sc}$  for the circuit of Fig. 1.

The Thevenin equivalent circuit can now be specified as

$$V_{Th} = V_{oc} = 8 \text{ V}, \quad R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{8 \text{ V}}{3.08 \text{ mA}} = 2.6 \text{ k}\Omega. \quad (9)$$

**SequelApp Exercises:** Find  $V_{Th}$ ,  $I_{sc}$ ,  $R_{Th}$  for each of the following cases (with other component values as shown in Fig. 1). Verify your answers using SequelApp.

1.  $R_2$  is changed from 2 k to 1 k.
2.  $I_s$  is changed from 5 mA to 2 mA.