

Op-amp circuits (EC_opamp_2.sqproj)

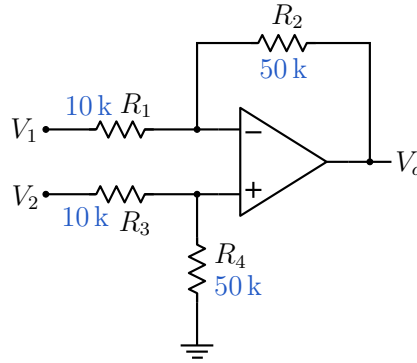


Figure 1: Difference amplifier circuit.

Question: In the difference amplifier shown in Fig. 1, $V_1 = V_C + V_m \sin \omega t$, $V_2 = V_C - V_m \sin \omega t$, with $V_C = 1, V$ and $V_m = 0.5 \text{ mV}$. The nominal values of the resistances are shown in the figure.

- (a) Find $V_o(t)$.
- (b) If R_1 is larger than its nominal value by 1%, how will $V_o(t)$ change?

Solution:

By superposition, the output voltage is given by

$$V_o = -\frac{R_2}{R_1} V_1 + \left(\frac{R_4}{R_3 + R_4} V_2 \right) \times \left(1 + \frac{R_2}{R_1} \right). \quad (1)$$

If $\frac{R_2}{R_1}$ is exactly equal to $\frac{R_4}{R_3}$, the circuit works as an ideal difference amplifier, with

$$V_o = \frac{R_2}{R_1} (V_2 - V_1). \quad (2)$$

With the help of the above equations, we can now answer the above questions.

- (a) In this case, we can use Eq. 2 and obtain

$$V_o = \frac{50 \text{ k}}{10 \text{ k}} \times (-2 V_m \sin \omega t) \quad (3)$$

$$= -(5 \text{ mV}) \sin \omega t. \quad (4)$$

(b) Since the resistances are not matched in this case, we need to use Eq. 2. Substituting component values in Eq. 2, we get

$$V_o = -\frac{50 \text{ k}}{10.1 \text{ k}} (V_C + V_m \sin \omega t) + \left(\frac{50 \text{ k}}{60 \text{ k}}\right) \left(1 + \frac{50 \text{ k}}{10.1 \text{ k}}\right) (V_C - V_m \sin \omega t) \quad (5)$$

$$= 8.25 \text{ mV} - (4.95 \text{ mV}) \sin \omega t. \quad (6)$$

SequelApp Exercises:

1. Find the output voltage in the following cases, assuming that the input voltages $V_1(t)$, $V_2(t)$, and the other circuit parameters remain the same as before.
 - (a) R_3 is changed to 10.1 k.
 - (b) R_2 is changed to 50.1 k.
2. For $V_1 = V_2 = 1 \text{ V}$ and R_2, R_3, R_4 equal to their nominal values, find R_1 for which $V_o = -12 \text{ mV}$.

Verify your answers using SequelApp.