

## Op-amp circuits (EC\_opamp\_3.sqproj)

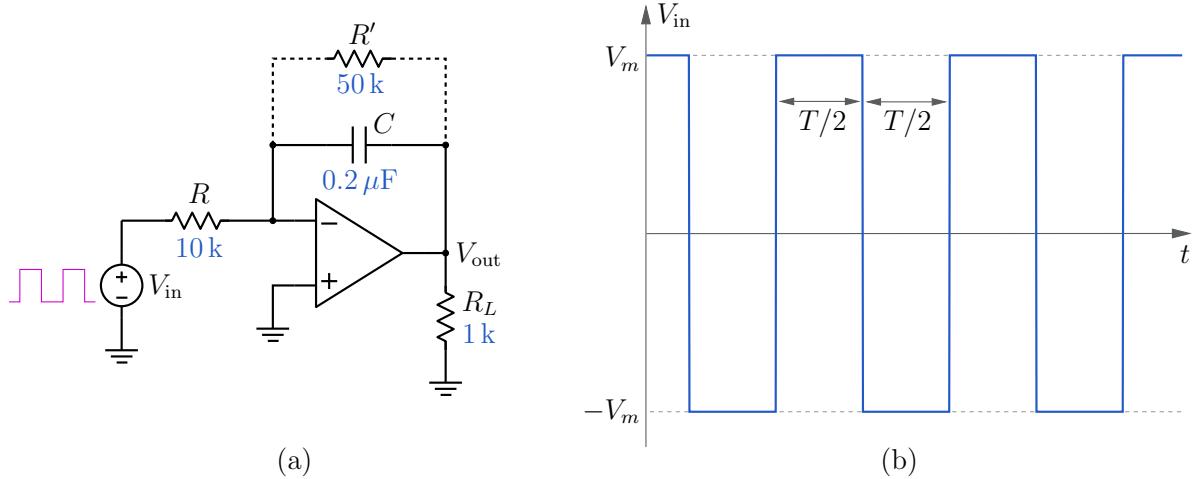


Figure 1: (a) Op-amp integrator circuit, (b) Input voltage waveform.

**Question:** In the integrator circuit shown in Fig. 1, the input voltage has  $V_m = 5\text{ V}$  and a frequency of 500 Hz. Plot the output waveform.

(Note that the resistor  $R'$  is required in a practical integrator circuit to prevent the op-amp from going into saturation because of op-amp offset voltage or input bias current.)

**Solution:**

The output voltage waveform for a square wave input is shown in Fig. 2. When  $V_{in}$  is equal to

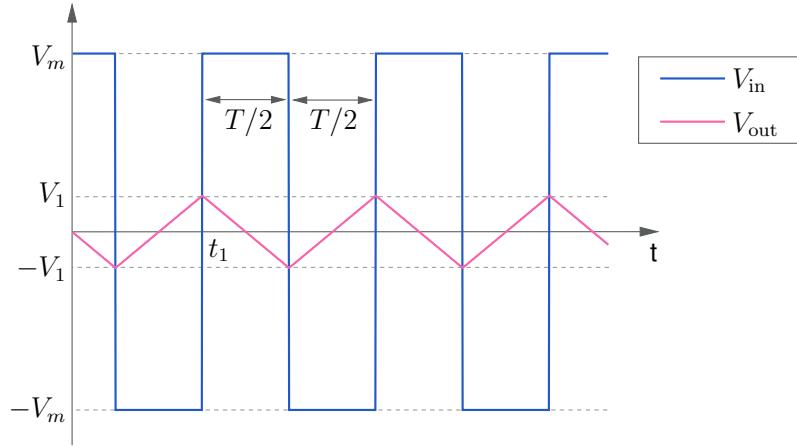


Figure 2: Input and output waveforms for the integrator of Fig. 1.

$+V_m$ , we have

$$V_{out} = -\frac{1}{RC} \int V_{in} dt = -\frac{1}{RC} \int V_m dt . \quad (1)$$

Integrating from  $t_1$  to  $t_1 + T/2$  (see Fig. 2), we get

$$-V_1 - V_1 = -\frac{1}{RC} V_m \frac{T}{2} \rightarrow 2V_1 = V_m \frac{T}{2RC}. \quad (2)$$

For the  $R$ ,  $C$ ,  $V_m$ ,  $T$  values specified above, we get  $V_1 = 1.25$  V.

**SequelApp Exercises:** With  $C = 0.1 \mu\text{F}$  and the same input voltage as specified above, what value of  $R$  will produce a 6 V peak-to-peak output voltage? Verify your answer using SequelApp.