

Phasors (EC\_phasors\_1.sqproj)

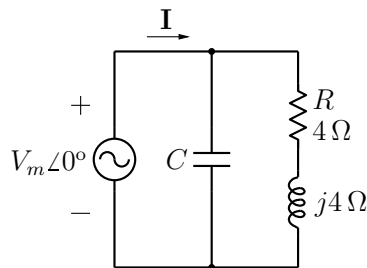


Figure 1: Phasor calculation example.

**Question:** In the circuit shown in the figure, the frequency is 50 Hz. Let  $\mathbf{I} = I_m \angle \theta$ . What value of  $C$  is required for  $\theta = 45^\circ$ ?

**Solution:**

The impedance as seen by the source is given by

$$\begin{aligned}
 \mathbf{Z}_{\text{eq}} &= (-jX_c) \parallel (4 + j4) \\
 &= \frac{X_c \angle -90^\circ \times 4\sqrt{2} \angle 45^\circ}{-jX_c + (4 + j4)} \\
 &= \frac{X_c \times 4\sqrt{2} \angle -45^\circ}{4 + j(4 - X_c)} \equiv \frac{a \angle -45^\circ}{b \angle \alpha},
 \end{aligned} \tag{1}$$

where  $\alpha$  is  $45^\circ$  and  $-90^\circ$  for  $X_c \rightarrow 0$  and  $X_c \rightarrow \infty$ , respectively. For  $\mathbf{I}$  to lead the source voltage by  $45^\circ$ ,  $\mathbf{Z}_{\text{eq}}$  must be of the form  $Z_m \angle -45^\circ$ , i.e.,  $\alpha$  in Eq. 1 must be  $0^\circ$ . This gives  $4 - X_c = 0 \rightarrow X_c = 4 \rightarrow \frac{1}{\omega C} = 4 \rightarrow C = \frac{1}{2\pi \times 50 \times 4} = 800 \mu\text{F}$ .

**SequelApp Exercises:** Find the value of  $C$  required for (a)  $\theta = 0^\circ$ , (b)  $\theta = 20^\circ$ .

Verify your answers using SequelApp.