

Phasors (EC\_phasors\_2.sqproj)

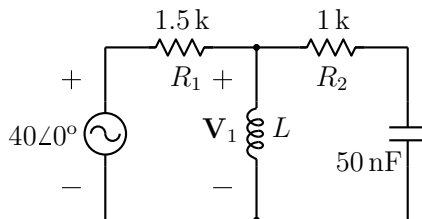


Figure 1: Phasor calculation example.

**Question:** In the circuit shown in the figure, the frequency is 1.6 kHz. With  $L = 100$  mH, find (a)  $\mathbf{V}_1$ , (b)  $P_{R2}$ , the average power dissipated in  $R_2$ .

**Solution:**

Using nodal analysis (see Fig. 1), we have

$$\frac{\mathbf{V}_s - \mathbf{V}_1}{R_1} = \frac{\mathbf{V}_1}{j\omega L} + \frac{\mathbf{V}_1}{R_2 - j/\omega C}. \quad (1)$$

With  $f = 1.6$  kHz, the impedances are evaluated as  $j\omega L = j1$  k $\Omega$  and  $-j/\omega C = -j2$  k $\Omega$ . Substituting

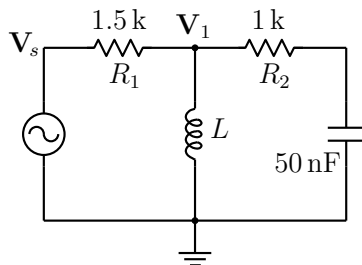


Figure 2: Nodal analysis of the circuit in Fig. 1.

in Eq. 1 and writing the currents in mA, we get

$$\frac{\mathbf{V}_s - \mathbf{V}_1}{1.5} = \frac{\mathbf{V}_1}{j1} + \frac{\mathbf{V}_1}{1 - j2}. \quad (2)$$

$$\rightarrow \frac{40}{1.5} = \mathbf{V}_1 (0.67 - j1 + (0.2 + j0.4)). \quad (3)$$

Solving the above equation, we get  $\mathbf{V}_1 = 25.4\angle 34.4^\circ$ , and  $P_{R2} = \frac{1}{2} \left| \frac{\mathbf{V}_1}{1 - j2} \right|^2 R_2 = 64.8$  mW.

**SequelApp Exercises:**

(a) Find  $L$  for which  $P_{R2}$  is half of the value obtained above.

(b) Find the corresponding  $\mathbf{V}_1$ .

Verify your answers using SequelApp.