

Phasors (EC_phasors_3.sqproj)

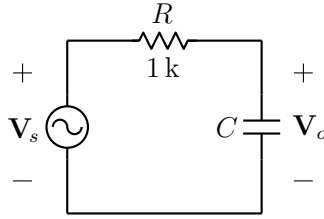


Figure 1: Phasor calculation example.

Question: In the circuit shown in the figure, the frequency is 1 kHz, and the source voltage is 1∠0 V.

- Find C for which the output voltage has an amplitude of 0.9 V. What is $\angle \mathbf{V}_o$ in this case?
- Find C for which the output voltage lags \mathbf{V}_s by 60° . What is $|\mathbf{V}_o|$ in this case?
- For (a) and (b), compute the time difference between the zero crossings of $V_s(t)$ and $V_o(t)$.
- Draw (to scale) a phasor diagram corresponding to the KVL equation.

Solution:

The output voltage is given by

$$\mathbf{V}_o = \frac{1}{R + \frac{1}{j\omega C}} \times \mathbf{V}_s = \frac{1}{1 + j\omega RC} \times \mathbf{V}_s = \frac{1}{1 + j\omega RC} \times 1\angle 0. \quad (1)$$

- (a) For $|\mathbf{V}_o| = 0.9$ V, we need

$$\frac{1}{\sqrt{1 + (\omega RC)^2}} = 0.9 \rightarrow C = 77 \text{ nF}, \text{ and in this situation, } \angle \mathbf{V}_o = -\tan^{-1} \omega RC = -25.8^\circ.$$

- (b) For $\angle \mathbf{V}_o = -60^\circ$, we need

$$-\tan^{-1} \omega RC = -60^\circ \rightarrow \omega RC = \tan 60^\circ = \sqrt{3} \rightarrow C = 276 \text{ nF},$$

$$\text{and in this situation, } |\mathbf{V}_o| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + 3}} = 0.5.$$

- (c) Let Δt be the time difference between the zero crossings of $V_s(t)$ and $V_o(t)$. Then we have

$$\frac{|\Delta t|}{T} = \frac{|\Delta \phi|}{2\pi} \rightarrow |\Delta t| = \frac{25.8^\circ}{360^\circ} \times 1 \text{ ms} = 72 \mu\text{s} \text{ in (a), and } |\Delta t| = \frac{60^\circ}{360^\circ} \times 1 \text{ ms} = 167 \mu\text{s} \text{ in (b).}$$

SequelApp Exercises:

- (a) Find C for which the output voltage has an amplitude of 0.7 V. What is $\angle \mathbf{V}_o$ in this case?
- (b) Find C for which the output voltage lags \mathbf{V}_s by 30° . What is $|\mathbf{V}_o|$ in this case?
- (c) For (a) and (b), compute the time difference between the zero crossings of $V_s(t)$ and $V_o(t)$.

Verify your answers using SequelApp (in frequency domain as well as time domain).