

Phasors (EC_phasors_4.sqproj)

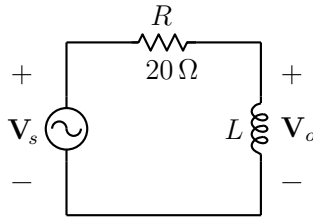


Figure 1: Phasor calculation example.

Question: In the circuit shown in the figure, the frequency is 50 Hz, and $\mathbf{V}_s = V_m \angle 0$.

- Find L for which $\frac{|\mathbf{V}_o|}{|\mathbf{V}_s|} = 0.8$. What is $\angle \mathbf{V}_o$ in this case?
- Find L for which the output voltage leads \mathbf{V}_s by 25° . What is $|\mathbf{V}_o|/|\mathbf{V}_s|$ in this case?
- For (a) and (b), compute the time difference between the zero crossings of $V_s(t)$ and $V_o(t)$.
- Draw (to scale) a phasor diagram corresponding to the KVL equation.

Solution:

The magnitude and phase of the output voltage are given by

$$|\mathbf{V}_o| = |\mathbf{V}_s| \times \left| \frac{j\omega L}{R + j\omega L} \right| = |\mathbf{V}_s| \times \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} = |\mathbf{V}_s| \times \frac{\omega L/R}{\sqrt{1 + (\omega L/R)^2}}. \quad (1)$$

$$\angle \mathbf{V}_o = \angle \mathbf{V}_s + \pi/2 - \tan^{-1} \left(\frac{\omega L}{R} \right). \quad (2)$$

- (a) Let us denote $\omega L/R$ by x . For $|\mathbf{V}_o| = 0.8 \times |\mathbf{V}_s|$ we need $\frac{x}{\sqrt{1+x^2}} = 0.8$

$$\rightarrow x = \frac{\omega L}{R} = \frac{4}{3} \rightarrow L = 84.9 \text{ mH, and in this situation,}$$

$$\angle \mathbf{V}_o = \angle \mathbf{V}_s + \pi/2 - \tan^{-1} x = \angle \mathbf{V}_s + 36.8^\circ.$$

- (b) For $\angle \mathbf{V}_o$ to lead $\angle \mathbf{V}_s$ by 25° , we need

$$90^\circ - \tan^{-1} x = 25^\circ \rightarrow x = \frac{\omega L}{R} = \tan 65^\circ \rightarrow L = 136 \text{ mH,}$$

$$\text{and in this situation, } \frac{|\mathbf{V}_o|}{|\mathbf{V}_s|} = \frac{1}{\sqrt{1+x^2}} = 0.9.$$

(c) Let Δt be the time difference between the zero crossings of $V_s(t)$ and $V_o(t)$. Then we have

$$\frac{|\Delta t|}{T} = \frac{|\Delta\phi|}{2\pi} \rightarrow |\Delta t| = \frac{36.8^\circ}{360^\circ} \times 20 \text{ ms} = 2 \text{ ms in (a), and } |\Delta t| = \frac{25^\circ}{360^\circ} \times 20 \text{ ms} = 1.4 \text{ ms in$$

(b).

SequelApp Exercises:

(a) Find L for which $\frac{|\mathbf{V}_o|}{|\mathbf{V}_s|} = 0.5$. What is $\angle \mathbf{V}_o$ in this case?

(b) Find L for which the output voltage leads \mathbf{V}_s by 45° . What is $\frac{|\mathbf{V}_o|}{|\mathbf{V}_s|}$ in this case?

(c) For (a) and (b), compute the time difference between the zero crossings of $V_s(t)$ and $V_o(t)$.

Verify your answers using SequelApp (in frequency domain as well as time domain).