

RC circuits (EC\_rc\_2.sqproj)

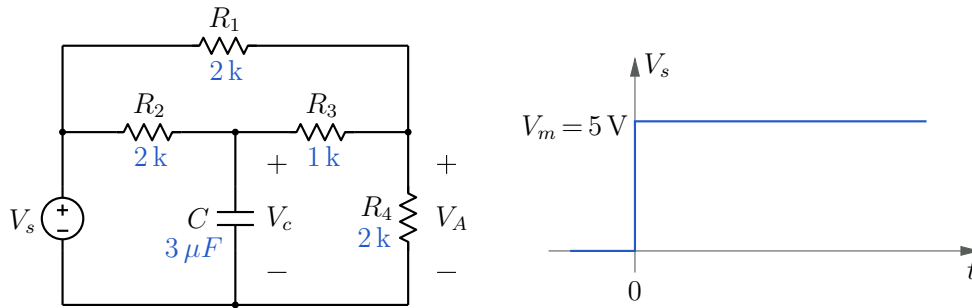


Figure 1: RC circuit with a step input.

**Question:** For the circuit shown in Fig. 1, find the following.

- (a) time constant
- (b)  $V_c(0^-)$  and  $V_A(0^-)$
- (c)  $V_c(0^+)$  and  $V_A(0^+)$
- (d)  $V_c(\infty)$  and  $V_A(\infty)$

Using the above values, plot  $V_c(t)$  and  $V_A(t)$ .

**Solution:**

- (a) The circuit time constant is given by  $\tau = R_{Th}C$ , where  $R_{Th}$  is the Thevenin equivalent resistance seen by the capacitor. To obtain  $R_{Th}$ , we deactivate the voltage source and find the resistance seen from the capacitor, as shown in Fig. 2. After simplifying the circuit, we get

$$R_{Th} = R_2 \parallel [R_3 + (R_1 \parallel R_4)]. \quad (1)$$

For the component values given in Fig. 1, we get  $R_{Th} = 1 \text{ k}$ , and  $\tau = R_{Th}C = 3 \text{ msec}$ . We can expect the transients to vanish after about  $5\tau = 15 \text{ msec}$ .

- (b) Since the source voltage has been  $0 \text{ V}$  for a long time before  $t = 0$ , we have  $V_c(0^-) = V_A(0^-) = 0 \text{ V}$ .

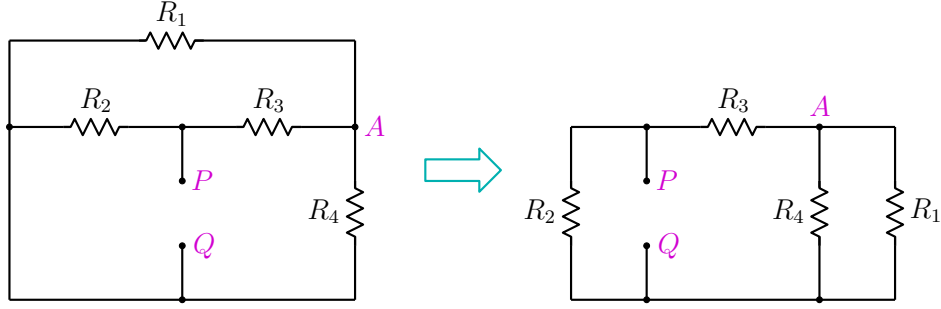


Figure 2: Calculation of the Thevenin resistance seen by the capacitor in the circuit of Fig. 1.

- (c) Since the capacitor voltage cannot change abruptly between  $t=0^-$  and  $t=0^+$ , we have  $V_c(0^+) = V_c(0^-) = 0$  V, as shown by a short circuit in Fig. 3. Writing KCL at node A, we get

$$\frac{V_m - V_A}{R_1} = \frac{V_A}{R_3} + \frac{V_A}{R_4} \rightarrow V_A \left[ \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} \right] = \frac{V_m}{R_1}, \quad (2)$$

where we have taken node Q as the reference node (0 V). Solving Eq. 2, we get  $V_A(0^+) = 1.25$  V.

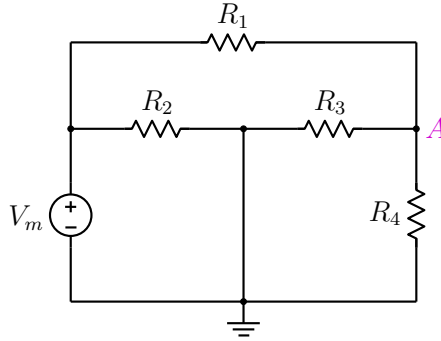


Figure 3: Circuit of Fig. 1 at  $t=0^+$ .

- (d) As  $t \rightarrow \infty$ , all voltages and currents become constant, the capacitor current  $i_c = C \frac{dV_c}{dt}$  becomes zero, and the capacitor can therefore be replaced with an open circuit, as shown in Fig. 4. Writing KCL at node A, we get

$$\frac{V_m - V_A}{R_1} + \frac{V_m - V_A}{R_2 + R_3} = \frac{V_A}{R_4} \rightarrow V_A \left[ \frac{1}{R_1} + \frac{1}{R_2 + R_3} + \frac{1}{R_4} \right] = V_m \left[ \frac{1}{R_1} + \frac{1}{R_2 + R_3} \right]. \quad (3)$$

Solving this equation, we get  $V_A(\infty) = 3.125$  V.  $V_c(\infty)$  can now be obtained as

$$V_c(\infty) = V_m \frac{R_3}{R_2 + R_3} + V_A(\infty) \frac{R_2}{R_2 + R_3}. \quad (4)$$

Substituting numerical values, we get  $V_c(\infty) = 3.75 \text{ V}$ .

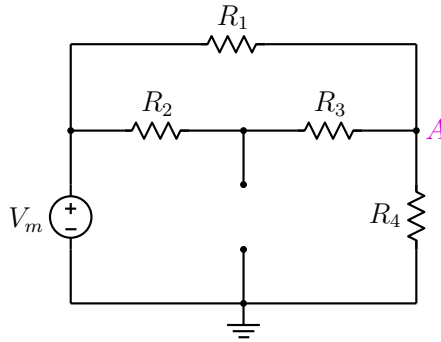


Figure 4: Circuit of Fig. 1 as  $t \rightarrow \infty$ .

Using the above results, we can now plot  $V_c(t)$  and  $V_A(t)$  (see Fig. 5).

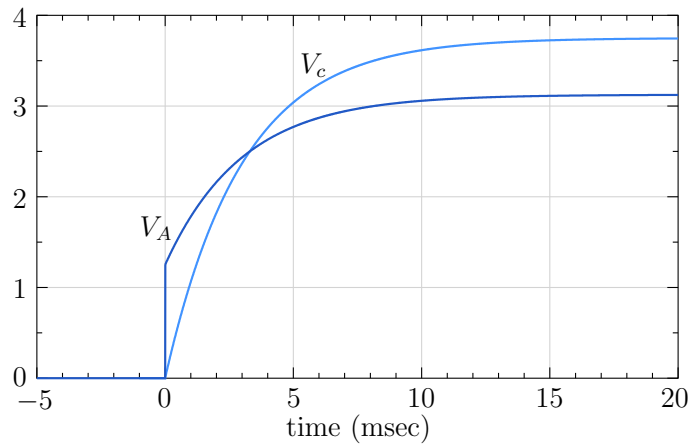


Figure 5:  $V_c(t)$ ,  $V_A(t)$  for the circuit of Fig. 1.

**SequelApp Exercises:** Repeat the above steps for the following situations, with other parameters the same as in Fig. 1. Verify your answers using SequelApp.

1.  $R_3 = 3 \text{ k}$ .
2.  $R_2 = 1 \text{ k}$ .