

Figure 1: RL circuit example.

**Question:** In the circuit shown in Fig. 1, the switch has been open for a long time and closes at  $t = 0$ . Plot  $i_L(t)$  and  $i_1(t)$ .

**Solution:**

First, let us look at the circuit at  $t = 0^-$  (see Fig. 2(a)). Since the switch has been closed for a long time, the circuit is in steady state, i.e., the currents and voltages are constant. Since  $v_L = L \frac{di_L}{dt}$  for an inductor,  $v_L(0^-)$  must be zero (since  $\frac{di_L}{dt} = 0$ ) which means that the inductor behaves like a short circuit, as shown in Fig. 2(b), and we find that

$$i_1(0^-) = i_L(0^-) = \frac{V_s}{R_3} = \frac{30 \text{ V}}{10 \Omega} = 3 \text{ A}.$$

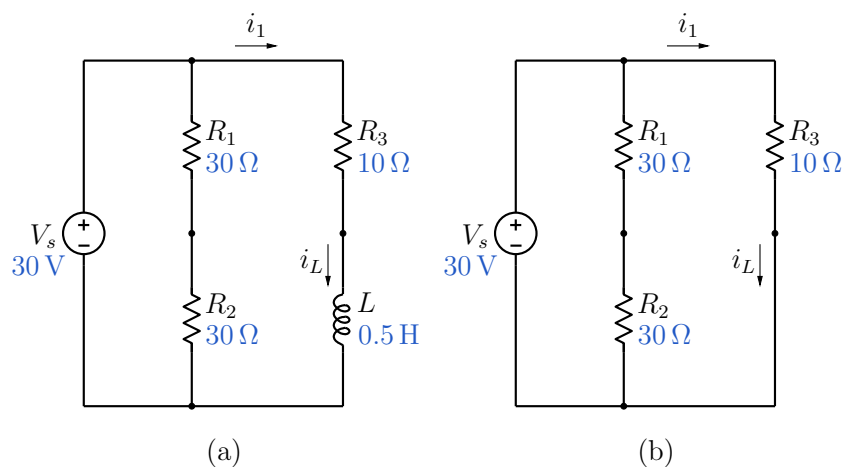


Figure 2: (a) Circuit of Fig. 1 at  $t = 0^-$ , (b) circuit after replacing the inductor with a short circuit.

The circuit after the switch closes at  $t = 0$  is shown in Fig. 3(a). The current  $i_L(0^+)$  must be

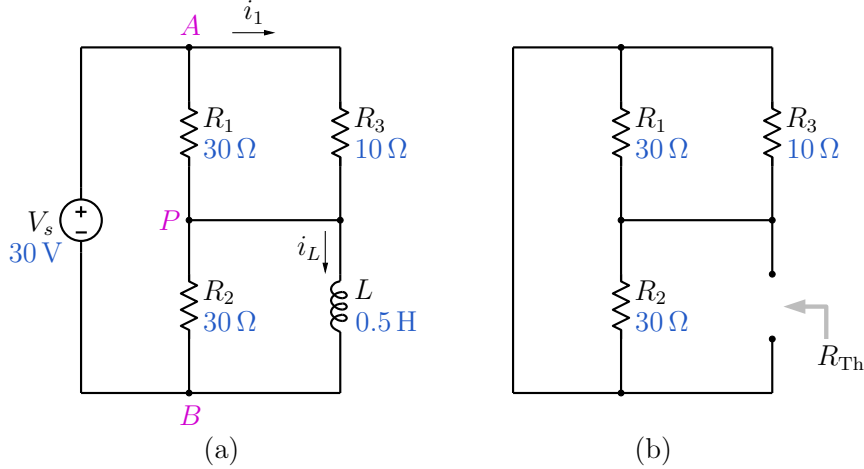


Figure 3: (a) Circuit of Fig. 1 for  $t > 0$ , (b) calculation of the Thevenin resistance seen by the inductor.

the same as  $i_L(0^-)$ ; otherwise, the inductor voltage  $L \frac{di_L}{dt}$  would become infinitely large, thus violating circuit equations. To obtain  $i_1(0^+)$ , we can first obtain the node voltage  $V_P$  (see Fig. 3 (a)), taking node  $B$  as the reference node (i.e.,  $V_B = 0$ ). KCL at node  $P$  can be written as

$$\frac{V_P - 0}{R_2} - \frac{V_A - V_P}{R_1} - \frac{V_A - V_P}{R_3} + i_L(0^+) = 0, \quad (1)$$

which gives  $V_P = 6$  V, and  $i_1(0^+) = \frac{V_A - V_P}{R_3} = 2.4$  A.

To find the circuit time constant, we find the Thevenin resistance as seen from the inductor (see Fig. 3 (b)). For this purpose, we deactivate the voltage source (replace it with a short circuit), and find  $R_{Th}$  to be  $(R_1 \parallel R_2 \parallel R_3) = 6 \Omega$ . The circuit time constant is  $\tau = 0.5 \text{ H} / 6 \Omega = 83.3$  msec. After the switch closes at  $t = 0$ , we expect all transients to vanish in about  $5\tau$  or 0.42 sec, and all currents and voltages would remain constant thereafter. Next, we need to obtain  $i_1(\infty)$  (i.e., the steady-state value of  $i_1$ ). The inductor can be replaced with a short circuit in the steady state (see Fig. 4), and we get

$$i_L(\infty) = \frac{V_s}{R_1 \parallel R_3} = 4 \text{ A}, \quad (2)$$

$$i_1(\infty) = i_L(\infty) \times \frac{R_1}{R_1 + R_3} = 4 \text{ A} \times \frac{30}{40} = 3 \text{ A}. \quad (3)$$

Putting together the above observations, we obtain the plots for  $i_L(t)$  and  $i_1(t)$  as shown in Fig. 5.

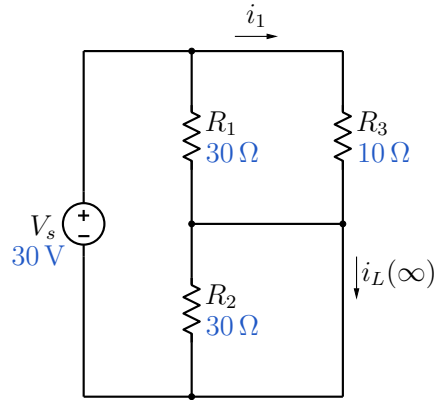


Figure 4: Calculation of  $i_L(\infty)$  for the circuit of Fig. 1.

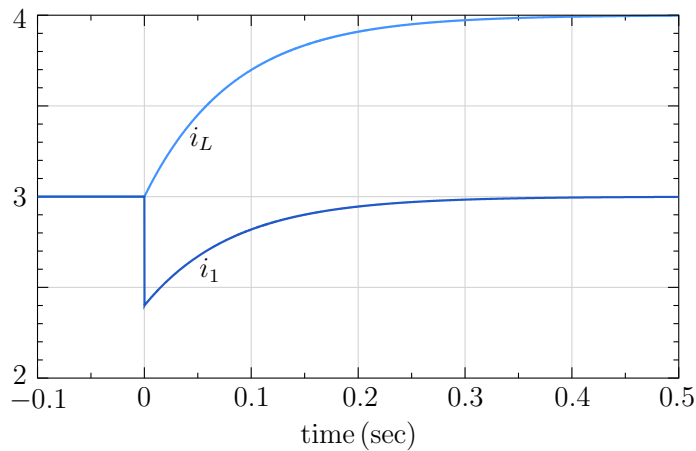


Figure 5:  $i_L$  and  $i_1$  versus time for the circuit of Fig. 1.

**SequelApp Exercises:** Repeat the above steps for the following situations, with other parameters the same as in Fig. 1. Verify your answers using SequelApp.

1. The switch opens (instead of closing) at  $t = 0$ .

(The above condition can be simulated by making `val1 = 1` and `val2 = 0`.)

2.  $R_2$  is changed to  $10\ \Omega$ ,  $R_3$  is changed to  $30\ \Omega$ , and the switch closes at  $t = 0$ .
3.  $R_2$  is changed to  $10\ \Omega$ ,  $R_3$  is changed to  $30\ \Omega$ , and the switch opens at  $t = 0$ .