

*RL circuits* (EC\_r1.2.sqproj)

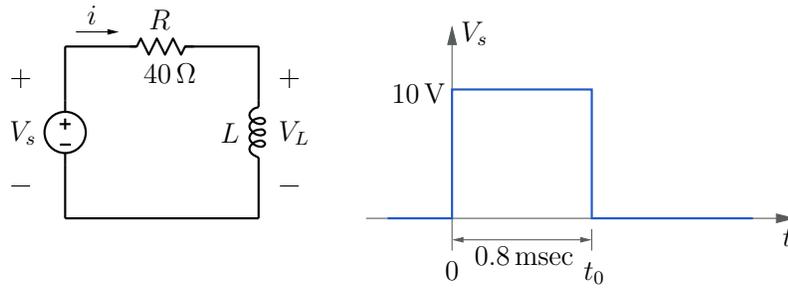


Figure 1: RL circuit example.

**Question:** In the circuit shown in Fig. 1,  $i$  is initially 0 A (i.e., before the input pulse is applied). The inductance  $L$  is 20 mH.

- Sketch  $i(t)$  and  $V_L(t)$ .
- Find the following values: (i)  $i(t_0^-)$ , (ii)  $i(t_0^+)$ , (iii)  $V_L(t_0^-)$ , (iv)  $V_L(t_0^+)$ .

**Solution:**

The waveforms  $i(t)$  and  $V_L(t)$  are shown in Fig. 2. The falling edge of the input voltage at  $t = t_0$  does not affect the circuit response for  $0 < t_0 < t$ . In other words, we can compute the response for a step change in  $V_s$  (see the dashed part in Fig. 2) rather than a pulse, and simply take the solution for  $0 < t_0 < t$ .

For this condition (i.e., a step change in  $V_s$ ), let  $i(t) = A_1 e^{-t/\tau} + B_1$ . Since  $i(t)$  is the inductor current, it does not change instantaneously, which means  $i(0^+) = i(0^-) = 0$  A.

As  $t \rightarrow \infty$ ,  $i \rightarrow \frac{10\text{ V}}{R} = 0.25$  A since the inductor voltage  $V_L = \frac{di}{dt}$  is zero in the steady state.

Using the above two conditions, we obtain  $A_1 = -0.25$ ,  $B_1 = 0.25$  (amps).

At  $t = t_0^-$ ,  $i(t)$  can now be evaluated as

$$i(t_0^-) = (-0.25)e^{-t_0/RC} + 0.25 = (-0.25)e^{-0.8\text{ msec}/0.5\text{ msec}} + 0.25 = 0.2\text{ A}.$$

$i(t_0^+)$  is the same as  $i(t_0^-)$  since the inductor current does not change instantaneously.

The  $V_L$  transient for  $0 < t_0 < t$  can be obtained in two ways: (i) by differentiating  $i(t)$ , since  $V_L = L \frac{di}{dt}$ , (ii) by computing  $V_L(t)$  for a step change in  $V_s$  to obtain  $V_L(t)$  for  $0 < t_0 < t$ .

Let us use the second approach, with  $V_L(t) = A_2 e^{-t/\tau} + B_2$ . At  $t = 0^+$ , we have  $V_s(0^+) = 10$  V and  $i(0^+) = 0$  A, giving  $V_L(0^+) = 10$  V. As  $t \rightarrow \infty$ ,  $V_L \rightarrow 0$ . These two conditions give  $A_2 = 10$  V,  $B_2 = 0$ , resulting in  $V_L(t) = (10\text{ V}) e^{-t/\tau}$ .

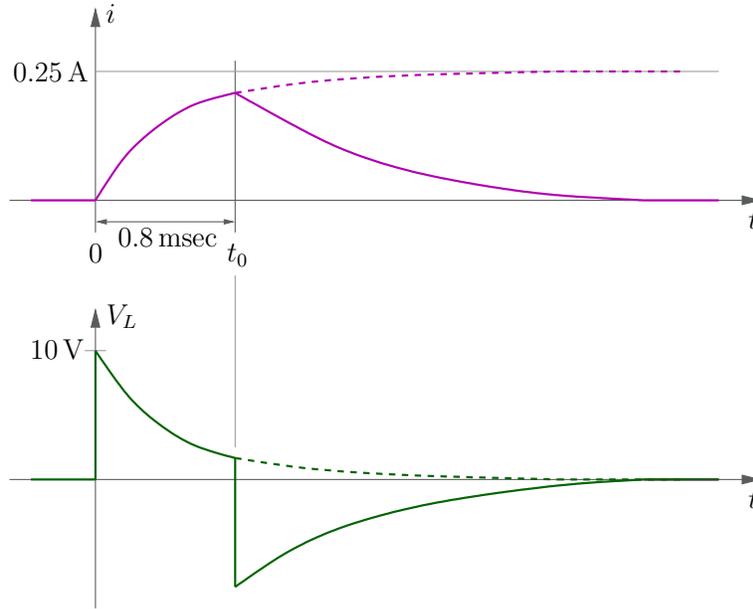


Figure 2: Schematic diagram showing  $i(t)$  and  $V_L(t)$  for the circuit of Fig. 1.

At  $t = t_0^-$ , the above expression gives  $V_L(t) = 2 \text{ V}$ .  $V_L(t_0^+)$  can be obtained as  $V_L(t_0^+) = V_s(t_0^+) - i(t_0^+) R = 0 - 0.2 \times 40 = -8 \text{ V}$ .

**SequelApp Exercises:** Find  $L$  for each of the following conditions:

1.  $i(t_0^-) = 0.1 \text{ A}$ .
2.  $V_L(t_0^-) = 5 \text{ V}$ .
3.  $V_L(t_0^+) = -6 \text{ V}$ .

Verify your answers using SequelApp.