

Op-amp circuits (EC_schmitt_1.sqproj)

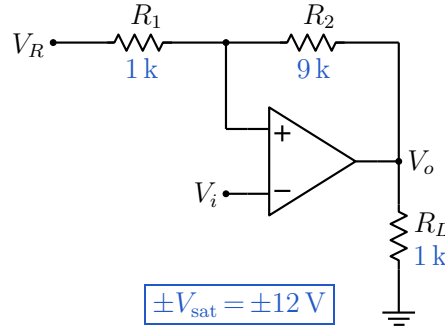


Figure 1: Schmitt trigger circuit.

Question: For the Schmitt trigger circuit shown in Fig. 1, plot V_o versus V_i for (a) $V_R = 0\text{ V}$, (b) $V_R = 5\text{ V}$.

Solution:

- (a) With $V_R = 0\text{ V}$, the circuit is the “standard” inverting Schmitt trigger with the V_o - V_i relationship shown in Fig. 2 (a). The output voltage changes from $+V_{\text{sat}}$ to $-V_{\text{sat}}$ at $V_i = V_{TH}$ (see Fig. 2 (b)), and it corresponds to $(V_+ - V_-)$ changing sign. To find V_{TH} , we need to find V_+ with $V_o = +V_{\text{sat}}$. In other words,

$$V_{TH} = V_+|_{V_o=+V_{\text{sat}}} = +V_{\text{sat}} \times \frac{R_1}{R_1 + R_2} = (+12\text{ V}) \times \frac{1\text{ k}\Omega}{10\text{ k}\Omega} = 1.2\text{ V}, \quad (1)$$

where the op-amp input current, which is negligibly small, has been ignored. Similarly,

$$V_{TL} = V_+|_{V_o=-V_{\text{sat}}} = -V_{\text{sat}} \times \frac{R_1}{R_1 + R_2} = (-12\text{ V}) \times \frac{1\text{ k}\Omega}{10\text{ k}\Omega} = -1.2\text{ V}. \quad (2)$$

- (b) With $V_R = 5\text{ V}$ (see Fig. 3 (a)), the basic operation of the circuit remains the same; however, the tripping points V_{TH} and V_{TL} get shifted, as shown in Fig. 3 (b). V_{TH} is found by calculating V_+ when $V_o = +V_{\text{sat}}$.

$$\begin{aligned} V_{TH} &= V_+|_{V_o=+V_{\text{sat}}} = +V_{\text{sat}} \times \frac{R_1}{R_1 + R_2} + V_R \times \frac{R_2}{R_1 + R_2} \\ &= (+12\text{ V}) \times \frac{1\text{ k}\Omega}{10\text{ k}\Omega} + (5\text{ V}) \times \frac{9\text{ k}\Omega}{10\text{ k}\Omega} \\ &= 5.7\text{ V}, \end{aligned} \quad (3)$$

where once again, we have neglected the op-amp input current. Similarly, V_{TL} can be found by evaluating V_+ when $V_o = -V_{\text{sat}}$.

$$\begin{aligned}
 V_{TL} &= V_+|_{V_o=-V_{\text{sat}}} = -V_{\text{sat}} \times \frac{R_1}{R_1 + R_2} + V_R \times \frac{R_2}{R_1 + R_2} \\
 &= (-12 \text{ V}) \times \frac{1 \text{ k}\Omega}{10 \text{ k}\Omega} + (5 \text{ V}) \times \frac{9 \text{ k}\Omega}{10 \text{ k}\Omega} \\
 &= 3.3 \text{ V}.
 \end{aligned} \tag{4}$$

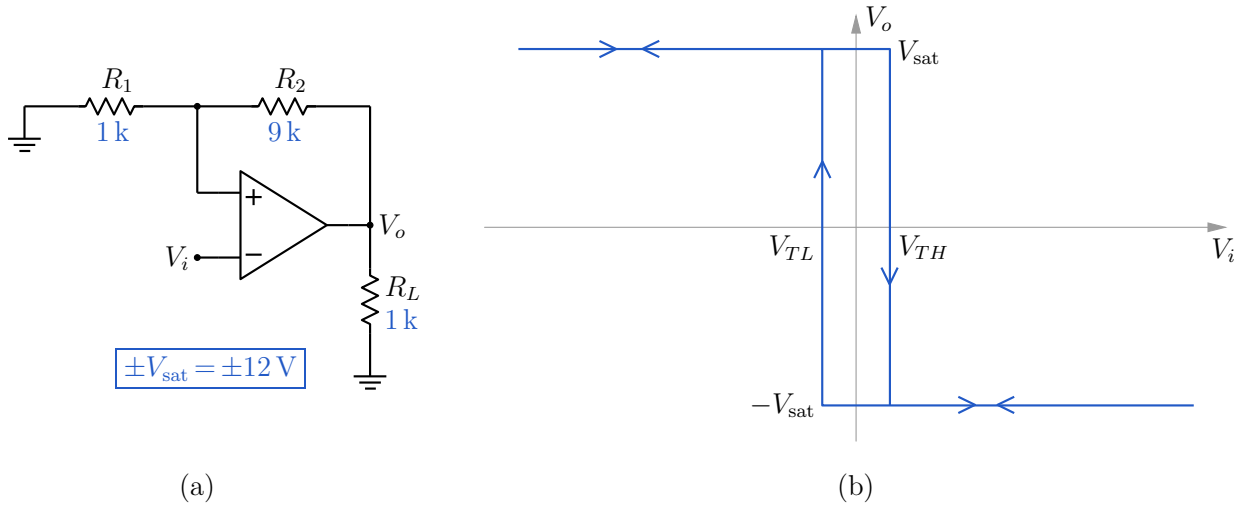


Figure 2: (a) Schmitt trigger of Fig. 1 with $V_R = 0 \text{ V}$, (b) V_o versus V_i relationship.

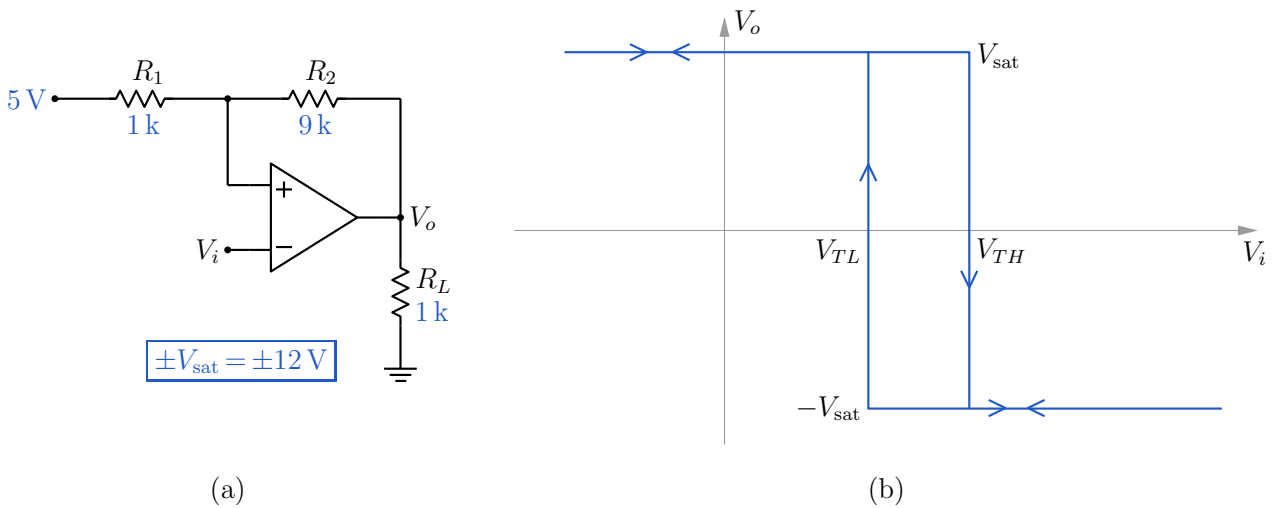


Figure 3: (a) Schmitt trigger of Fig. 1 with $V_R = 5 \text{ V}$, (b) V_o versus V_i relationship.

SequelApp Exercises:

1. For the Schmitt trigger of Fig. 1, find V_{TH} and V_{TL} in the following situations, other circuit parameters being the same as in the figure.
 - (a) $V_R = 2\text{ V}$.
 - (b) $V_R = -2\text{ V}$.
 - (c) $V_R = 5\text{ V}$, $R_1 = 4\text{ k}$.
2. With $V_{\text{sat}} = 12\text{ V}$ and $R_2 = 9\text{ k}$, find R_1 and V_R required to obtain $V_{TL} = 1\text{ V}$ and $V_{TH} = 3\text{ V}$.

Verify your answers using SequelApp.