

Department of Electrical Engineering, IIT Bombay  
**EE206 Digital Circuits: Tutorial Sheet III**  
Combinational Logic: MSI and LSI

1. **Priority Encoder** Given an Octal-to-Binary Encoder Chip with all input and output lines as shown in Figure 1(a). Using this chip, and only NOT, AND and OR gates, design an *Octal-to-Binary Priority Encoder*, whose required input and output lines are shown in Figure 1(b). Assume the

 


Figure 1: (a) The given Octal-to-Binary Chip, and (b) Input and Output lines for the desired Priority Encoder

availability of suitable multi-input AND and OR gates. Write down *all* boolean expressions, and show only important connections in the circuit. A *LINE ACTIVE* output is 1 when any of the inputs  $P_7 - P_0$  is 1, 0 otherwise. An *ENABLE* input causes the system to operate according to the desired functionality when  $ENABLE = 1$ , else is disabled when  $ENABLE = 0$ . A Priority Encoder operates on the principle that *more than one input*  $P_i$ ,  $0 \leq i \leq 7$  could be 1 at a time, unlike a normal Encoder. For a Priority Encoder, the output is a binary number, corresponding to the “highest”  $P_i$  that is 1 *i.e.*, the output corresponds to  $i$  such that  $P_i = 1$ ,  $P_j = 0 \forall i < j \leq 7$ .

2. **Combinational Circuit Design with Multiplexers** The input to a digital circuit are three signals  $A$ ,  $B$  and  $C$  (Note that  $\overline{A}$ ,  $\overline{B}$  and  $\overline{C}$  are *NOT* available). Logic 1 and 0 are available (*e.g.*, as  $V_{CC}$  and  $GND$ ). The output of the circuit is given to be  $f = \overline{A}B + \overline{A}\overline{B}\overline{C}$ . Implement the circuit using *only TWO* 2 : 1 *Multiplexer Modules* of the form shown in Figure 2(b) - do not use any other hardware.  $s$  is the select line. Data lines  $D_0$  and  $D_1$  are selected (*i.e.*, made the output  $Y$ ) when  $s = 0$  and 1, respectively.
3. **Decoders** Design a 8 : 256 decoder using 2 : 4 decoders, and SSI hardware chips (if required), both in a tree configuration, as well as in the coincident configuration. How would you compare the hardware requirements in the two cases ?

 


Figure 2: (a) The 3-input combinational circuit to be designed, and (b) A 2:1 Multiplexer Module.

4. **BCD-to-Decimal Decoder** Design a BCD-to-Decimal Decoder. The circuit should also handle the case when an invalid input combination occurs - all outputs should be made zero in this case.
5. **Circuit Design using Decoders** (*Drill Problem*), *Mano, Problem 5-18*  
A combinational circuit is defined by the following two functions:

(a)  $F_1(x, y) = \sum(0, 3)$

(b)  $F_2(x, y) = \sum(1, 2, 3)$

- Implement the circuit with a 2 : 4 decoder with an *ENABLE* input, and external NAND gates.
- Now, implement this with 4 : 1 multiplexers, and OR gate, and an inverter.

6. **Circuit Design using Decoders and Multiplexers** (*Drill Problem*), *Mano, Problems 5-17 and 5-24*

A combinational circuit is defined by the following three functions:

(a)  $F_1 = x'y' + xyz'$

(b)  $F_2 = x' + y$

(c)  $F_3 = xy + x'y'$

Design the circuit with a decoder and external gates.

7. **Circuit Design using Multiplexers** (*Drill Problem*), *Mano, Problem 5-26*

Implement a Full Adder circuit using multiplexers.

8. **ROM** *Mano, Problem 5-28*

*Prove* (using the representation of a number in a number system as a linear combination of powers of the base) that a  $32 \times 8$  ROM can be used to implement a circuit that generates the binary square of an input 5-bit number with  $B_0 = A_0$ , and  $B_1 = 0$ . Draw a block diagram of the circuit and list the first four and last four entries of the ROM truth table.