

Department of Electrical Engineering, IIT Bombay  
**EE206 Digital Circuits: Tutorial Sheet IV**  
Sequential Logic

1. **Clearing Concepts** Clearly explain the significance of an *asynchronous* clear input ( $\overline{CLEAR}$ ) to a positive edge-triggered D-Flip Flop shown in Figure 1(a).

 


Figure 1: (a) Positive Edge-Triggered D-Flip Flop with Asynchronous Clear, and (b) An example of a ripple counter

2. **Positively Edgy** Based on Mano, Problem 7-1 Draw the basic unit of a  $n$ -bit register consisting of positive edge-triggered D-Flip Flops. The functionalities in the registers are to be an asynchronous  $\overline{CLEAR}$  and a  $LOAD$  input - both common to all  $n$  Flip Flops. Now, modify this structure so that the system is a negative edge triggered system. You can use any SSI hardware for the task.
3. **Drill Problem, Mano, Problem 7-4** Design the sequential circuit whose state table is given below using a 2-bit register (constructed using D-Flip Flops), and combinational gates.

Present State		Input	Next State	
$A$	$B$	$x$	$A$	$B$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	0	1

4. **Out of sync?** Mano, Problem 7-18 The ripple counter shown in the Figure 1(b) uses Flip Flops that trigger on the negative edge transition of the  $CP$  input. Determine the count sequence of the counter. Is the counter self-starting? (A counter is said to be **self-starting** if it can start from any state, but eventually reaches the normal count sequence.)

## 5. Synchronous Sequential Circuit Design

- (a) **PQLiar Question** Consider a hypothetical “PL”-Flip Flop, shown in Figure 2(a), along with its *Excitation Table*. Derive the corresponding *Characteristic Table*. Note that this hypothetical PL-Flip

 


Figure 2: (a) PL-Flip Flop, and (b) Figure for the Counter

Flop has exactly 3 inputs  $P$ ,  $L$  and  $CP$ ; and exactly 2 outputs  $Q$  and  $\bar{Q}$ .

- (b) **A “Counter Example”** It is required to design a binary mod-5 Synchronous up-counter using PL-Flip Flops, as shown in Figure 2(b).  $Q_2Q_1Q_0$  changes as  $000 \rightarrow 001 \rightarrow 010 \dots$  ( $Q_2$  is the MSB,  $Q_0$  is the LSB), such that the machine always functions as an up-counter, and the only way a count can go down, is to 000.
- Write down the Excitation Table for the counter.
  - Obtain simplified SOP expressions for the inputs  $P_2$ ,  $L_2$ ,  $P_1$ ,  $L_1$ ,  $P_0$ ,  $L_0$  in terms of  $Q_2$ ,  $Q_1$ ,  $Q_0$ , and their complements.
  - Implement the combinational logic part of the Counter using a *Minimum* number of 2-input NAND gates *only*.

## 6. Mealy and Moore Machines

- (a) Consider the construction to convert a Mealy Machine  $M$  into its equivalent Moore Machine  $M'$  - this is just a construction, without a proof. Given that  $M$  enters arbitrarily numbered states  $q_0, q_1, \dots, q_n$  on inputs  $a_1, a_2, \dots, a_n$ , and emits outputs  $b_1, b_2, \dots, b_n$ , then  $M'$  should enter states  $q'_0, q'_1, \dots, q'_n$  on the same inputs, and emit the same outputs. Specify  $q'_0, q'_1, \dots, q'_n$ . Next, prove the above statement by induction on the length of the input string.
- (b) Convert the Mealy Machine in Figure 3(a) to its equivalent Moore model.

## 7. DFAs Explain your answer in each case. Consider $\Sigma = \{0, 1\}$ .

- (a) Construct a DFA to accept strings starting with 1 and representing numbers divisible by 3. (*e.g.*, string 11 would be accepted, whereas strings 0, 00011 and 10 would not: the MSB of these strings is the leftmost bit and the LSB is the rightmost one. The above strings represent the decimal numbers 3, 0, 3 and 2, respectively).
- (b) *Hopcroft & Ullman, Exercise 2-5a* Construct a DFA to accept the set of all strings ending in 00.
- (c) *Hopcroft & Ullman, Exercise 2-5c* Construct a DFA to accept the set of all strings such that every block of 3 consecutive symbols contains at least two 0s.

8. **Being stingy: State Minimization** Consider the DFA shown in Figure 3(b). Write down the 5-tuple Finite State Machine definition for this

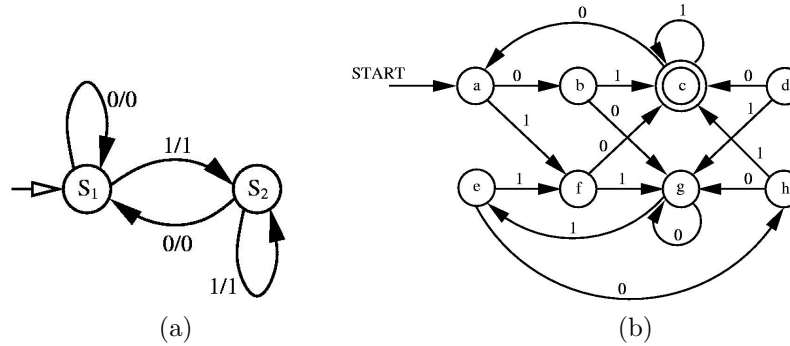


Figure 3: (a) Mealy Machine for conversion to Moore, and (b) DFA for State Minimization

DFA. Now, perform the  $k$ -Equivalence State Minimization Algorithm on this DFA, and show the steps involved.

9. **AHPL Question 1** *Hill & Peterson: Digital Systems, Problem 4-11:* Construct a detailed logic block diagram of the hardware realization of the control and data units specified by the following AHPL description, where **a** and **b** are flip flops, **x** is an input, and **z** is a single output line.
- ```

1  a ← x ∨ b
2  b ← x
   → (a, ā) / (1, 3)
3  z = 1; b ← x ⊕ b
   → (1)
    
```

Use the convention of one Flip Flop per control step, show the hardware implementation of *both the Data Unit, as well as the Control Unit*. For reference, a sample AHPL program line embodies all concepts required for the above implementation:

```

17 A ← B;
   → (l1, l2) / (3, 19)
    
```

Here, the first part is the data transfer part, which involves a transfer from register **B** to register **A** (Had **B** been a bus, the  $\leftarrow$  would have been replaced by  $=$ ). The second part of the statement is the control portion, which involves a conditional branch to statements numbered 3 and 19, based on the logical expressions  $l_1$  (e.g.,  $\bar{c} \vee d$ ) and  $l_2$  being 1, respectively. (Unconditional branch to 4 represented as:  $\rightarrow 4$ ). An AHPL statement can have a blank control or branch part also.

10. **AHPL Question 2** *Hill & Peterson: Digital Systems, Problem 4-19:* A digital system has an 8-bit vector **X** of input lines together with another input line **ready**. The system will have two output lines **z** and **ask**. Following each one period level placed on line **ask**, a new vector will be available on lines **X**. the availability of such a vector will be signaled by a one-period level on the line **ready**. Each time an input vector is exactly the same as either of the two previous input vectors, the output **z** should be 1 for four clock periods prior to another signal on link **ask**. The line **z** should be 0 at all other times. Write an AHPL sequence describing this digital system. Define the data registers as required.