
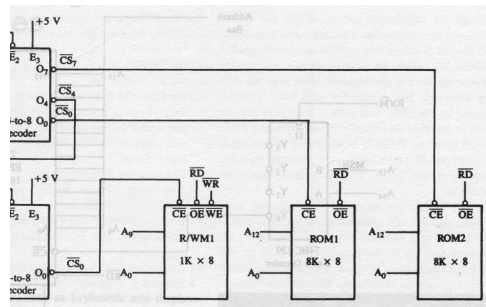


Department of Electrical Engineering, IIT Bombay
**EE309 Computer Organization, Architecture and
 Microprocessors: Tutorial Sheet II**
The 8085: Hardware and Interfacing

 1. Consider Figure 1 (Gaonkar, Chapter 3). \overline{CS} and \overline{CE} denote ‘Chip Select’ and ‘Chip Enable’. \overline{OE} and \overline{WE} enable the output buffer of a memory chip for a read operation, and enable a write, respectively.



- (a) Specify the memory addresses of ROM1, ROM2 and R/W/M1.
 (b) Eliminate the second decoder and connect \overline{CS}_4 to \overline{CE} of the R/W/M1, and identify its memory map and foldback memory. Normally, one considers a memory range by considering all ‘don’t care’ lines as 0s. The rest of the memory space is the foldback memory.
2. Consider Figure 2 (Gaonkar, Chapter 3).




- (a) Identify the address range of the memory chip.
 (b) Connect Y_1 to the \overline{CE} of the memory chip in place of Y_0 , and identify the address range of the memory chip.

3. (Gaonkar, Chapter 4)


- Explain why a latch is used for an output port, and a tristate buffer is used for an input port.
- What 8085 control signals are needed for memory-mapped I/O ?
- Can the μP differentiate between the cases when it is reading from a memory-mapped input port, or reading from memory ?

4. Consider Figure (Gaonkar, Chapter 4).

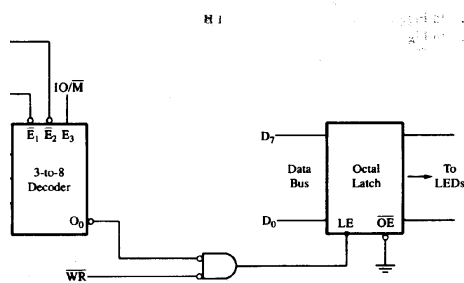


- Identify the port addresses.
- If \overline{OE} is connected directly to the \overline{WR} signal and the output of the decoder is connected to the latch enable (through an inverter), can you display a byte at the output port ? Explain your answer.

5. Consider Figure (Gaonkar, Chapter 4).

 


- Justify that the arrangement shown represents peripheral-mapped (Isolated) I/O.
- What is the port address if all the don't care address lines are assumed to be at logic 0 ?

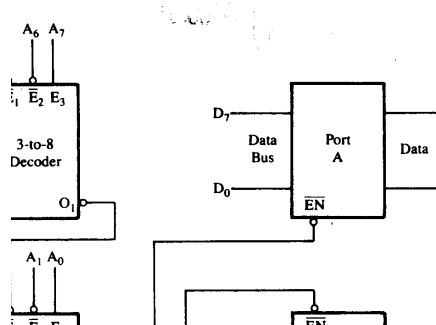6. Consider Figure (Gaonkar, Chapter 4). Identify ports A and B as input



or output ports. What are the addresses of ports A and B ?

7. Mem(I/O)orable Question

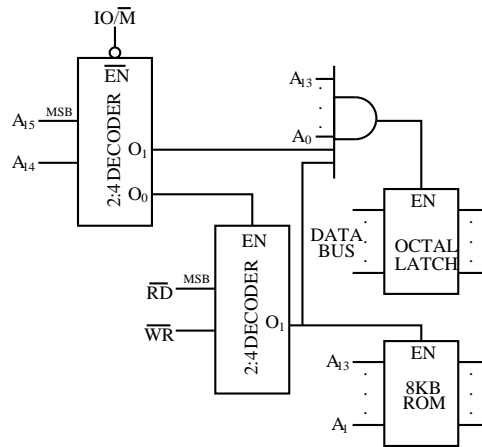

- (a) Identify the memory map of the ROM chip, and its foldback memory.
- (b) Identify the port as an Input port or an Output Port. Is this I/O Isolated (Peripheral-mapped), or Memory-mapped ?