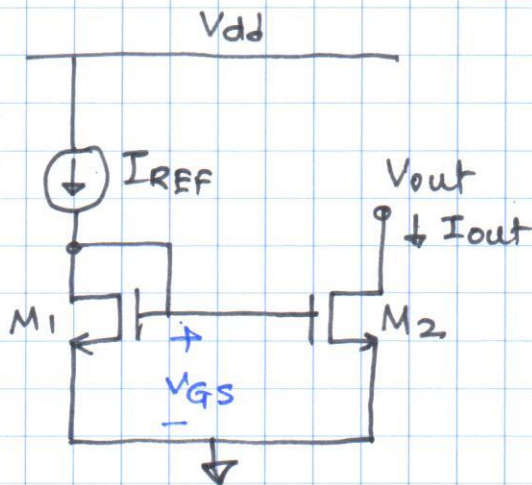



23MAR2020

Simple Current Mirror (Revisit)



$$\frac{I_{out}}{I_{REF}} = \frac{(W/L)_2 (1 + \lambda_2 V_{out})}{(W/L)_1 (1 + \lambda_1 V_{GS})}$$

* Random Process Variations

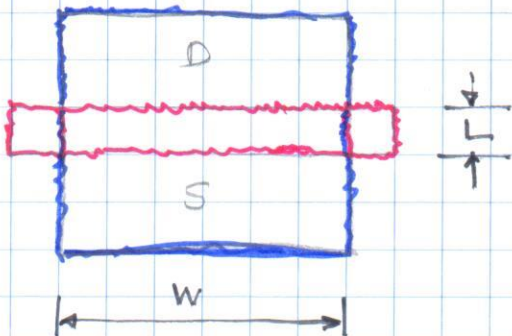

Edges defining transistor gate region - Noisy due to photolithography.

σ - standard deviation.
 σ^2 - variance

$$I \propto (W/L) \Rightarrow \left(\frac{\sigma_I}{I}\right)^2 \propto \left(\frac{\sigma_W}{W}\right)^2 + \left(\frac{\sigma_L}{L}\right)^2$$

If $W \gg L$ (Typ for ~~analog~~ analog design) W & L indep. variables.


$$\left(\frac{\sigma_I}{I}\right)^2 \propto \left(\frac{\sigma_L}{L}\right)^2$$

To be more accurate you have to consider V_T mismatches, μ , C_{ox} etc

* Systematic Errors } Layout Errors (different orientation)
 Design Errors (different VDS for example)

Each defining edge (dimension) can have errors.

Consider channel length L

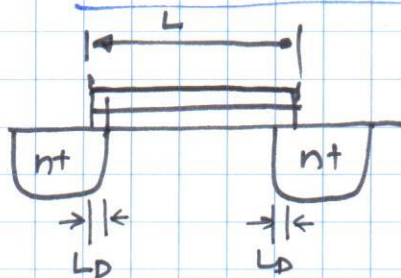


L_D - due to lateral diffusion of S/D

$$L_{eff} = L_{drawn} - 2L_D$$


$\Rightarrow L_{drawn}$ & $N L_{drawn}$ will not give you scaling by N for L_{eff} .

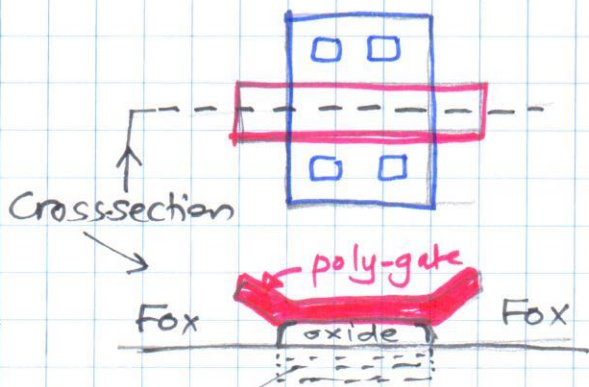Consider Channel Width W - Mos Cross-section



Desired W

$L_{actual} = W + \Delta W$

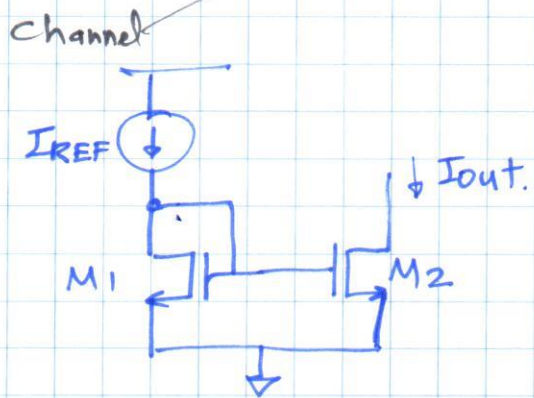

Desired $I_{out} = N I_{REF}$ integer

Case I $M_1 = W/L$; $M_2 = NW/L$

$$\frac{I_{out}}{I_{REF}} = \underbrace{\left(\frac{NW + \Delta W}{L + \Delta L} \right)}_{M_2} \times \underbrace{\left(\frac{L + \Delta L}{W + \Delta W} \right)}_{M_1}$$

$$= \frac{NW + \Delta W}{W + \Delta W}$$

Case II $M_1 = W/L$; $M_2 = N \text{ devices of } W/L \Rightarrow \frac{I_{out}}{I_{REF}} = \frac{NW + N\Delta W}{W + \Delta W} = N$

Differential Amplifiers

Why differential amplifiers.

- ⊙ ECG example
- ⊙ Detecting very small (differential) signal in presence of very large (common-mode) signal.
- ⊙ Whisper in presence of screams.

Concept

Single-Ended (SE) Signal





$$V_{SE} = V_c \cos \omega_c t + V_d \cos \omega_d t$$

large undesired signal (mV)

Small desired signal (μV)

Differential (DE) Signal

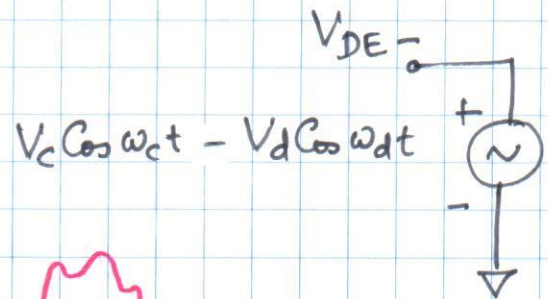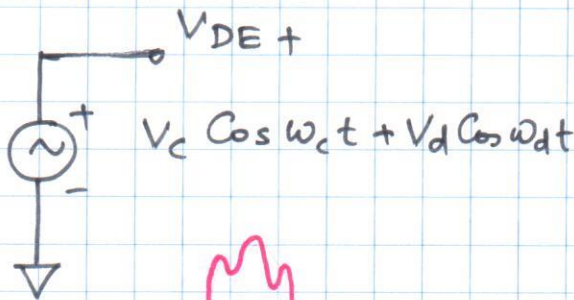


Large common-mode signal

Small differential signal

- ex. due to 50 Hz supply hum,

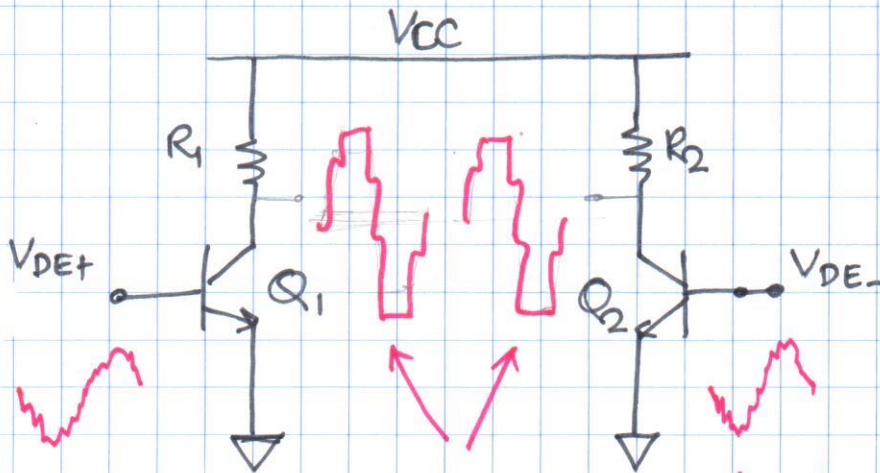
Two identical amplifiers driven by V_{DE+} & V_{DE-}
(Pseudo-Differential)



Clipping of signal due to large common-mode signal

Goal: Amplify only Differential Signal (desired)
— Reject common-mode signal (undesired).


Basic Differential Pair — innovation

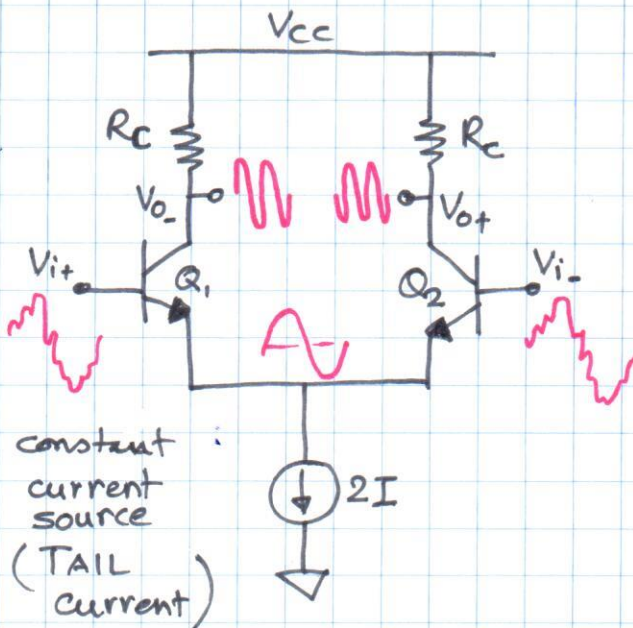

common-mode signal appears across current source.

Only Differential Signal is amplified at o/p.

Qualitative understanding of Diff. pair

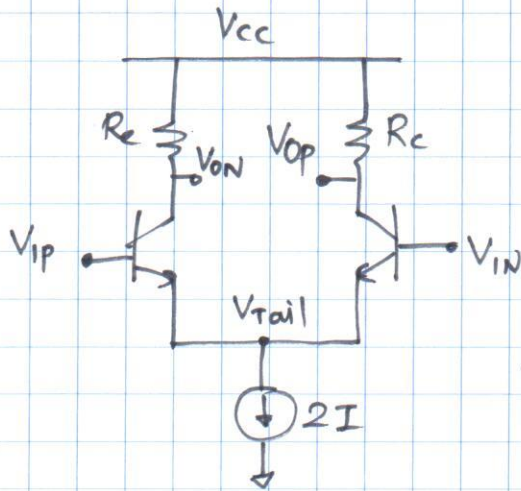

$$V_{CM} = \frac{V_{IP} + V_{IN}}{2}$$

$$V_{DM} = \frac{V_{IP} - V_{IN}}{2}$$


$$\Rightarrow V_{IP} = V_{CM} + \frac{V_{DM}}{2}$$

$$V_{IN} = V_{CM} - \frac{V_{DM}}{2}$$

"only"

When V_{CM} is applied to both i/p's

Q_1 & Q_2 each carry I .

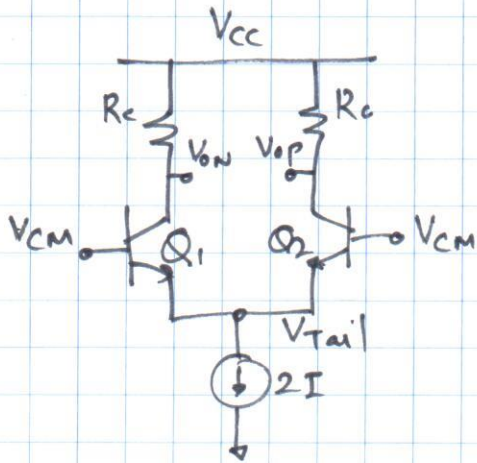

$$V_{OP} = V_{ON} = V_{CC} - I R_C$$

Indep. of V_{CM}

$$V_{Tail} = V_{CM} - V_{BE}$$

When V_{DM} is applied. (on top of V_{CM})


$$V_{OP} = V_{CC} - I R_C + g_m \frac{V_{DM}}{2} \cdot R_C$$

$$V_{ON} = V_{CC} - I R_C - g_m \frac{V_{DM}}{2} \cdot R_C$$

$$V_{OP} - V_{ON} = g_m V_{DM} \cdot R_C$$

$$\frac{V_{out\,diff}}{V_{in\,diff}} = \frac{V_{OP} - V_{ON}}{V_{DM}} = g_m R_C$$

↑
Transcond of each transistor

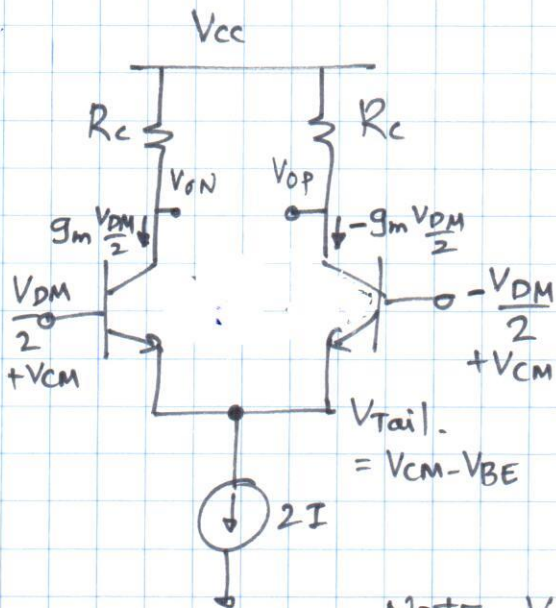

NOTE = V_{tail} is indep. of V_{DM} — virtual ground.