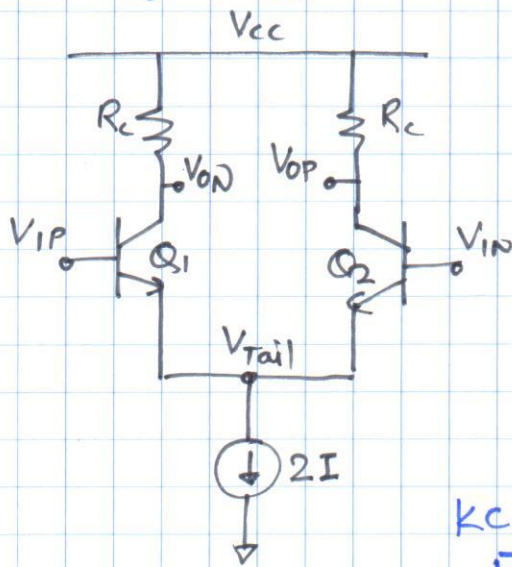


24MAR2020

Large signal Analysis (Bipolar Diff pair)  
ignore  $r_o$  & base current



$$V_{IP} - V_{BE1} = V_{Tail} = V_{IN} - V_{BE2}$$

$$V_{IP} - V_{IN} = V_{BE1} - V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$V_{IP} - V_{IN} = V_T \ln \left( \frac{I_{C1}}{I_{C2}} \right) \quad \text{--- (1)}$$

KCL @ VTAIL.

$$I_{C1} + I_{C2} = 2I \quad \text{--- (2)}$$

from (1)  $I_{C1} = I_{C2} \cdot \exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right)$

Substitute in (2)

$$I_{C2} \exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right) + I_{C2} = 2I$$


$$I_{C2} = \frac{2I}{1 + \exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right)} \quad \text{--- (3)}$$

$$I_{C1} = \frac{2I \cdot \exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right)}{1 + \exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right)}$$

$$\frac{V_{OP} - V_{ON}}{2I R_c} = -R_c (I_{C2} - I_{C1}) = R_c (2I) \frac{\exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right) - 1}{\exp\left(\frac{V_{IP} - V_{IN}}{V_T}\right) + 1}$$

$$= 2R_c I \cdot \tanh\left(\frac{V_{IP} - V_{IN}}{2V_T}\right)$$
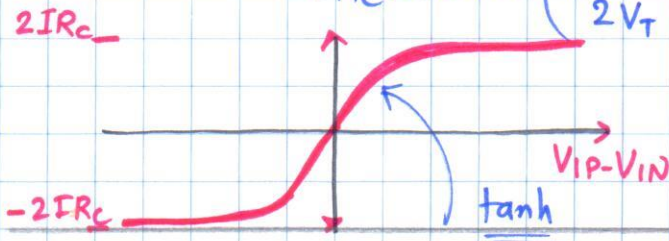
$$\begin{aligned} &\rightarrow -2I R_c (V_{IP} - V_{IN}) \ll 0 \\ &\rightarrow +2I R_c (V_{IP} - V_{IN}) \gg 0 \end{aligned}$$




Note: No inversion since labling of  $V_{OP}$  &  $V_{ON}$  already is inverted.
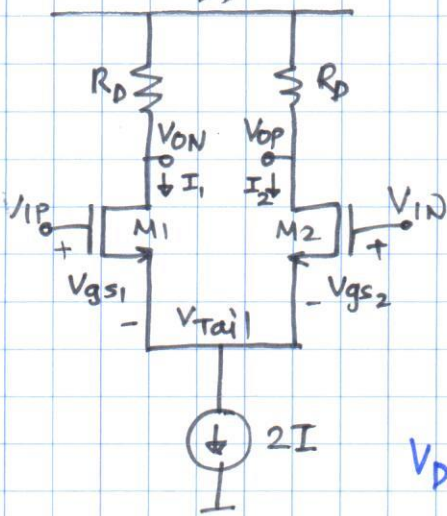
# Large Signal Analysis (MOSFET Diff. Pair)

ignore  $r_o$  & Body effect  
 $M_1$  &  $M_2$  are matched.

$$k_n = \mu_n C_{ox} \left( \frac{W}{L} \right)$$



$$I_1 = \frac{k_n}{2} (V_{gs1} - V_{TH})^2 \rightarrow V_{gs1} = V_{TH} + \sqrt{\frac{2I_1}{k_n}}$$

$$I_2 = \frac{k_n}{2} (V_{gs2} - V_{TH})^2 \rightarrow V_{gs2} = V_{TH} + \sqrt{\frac{2I_2}{k_n}}$$

$$V_{DM} = V_{IP} - V_{IN} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_1}{k_n}} - \sqrt{\frac{2I_2}{k_n}}$$

$$\begin{aligned} \text{also } I_1 + I_2 &= 2I \\ I_1 - I_2 &= \Delta I \end{aligned} \Rightarrow \begin{aligned} I_1 &= I + \frac{\Delta I}{2} \\ I_2 &= I - \frac{\Delta I}{2} \end{aligned}$$

$$V_{DM}^2 = \frac{2I_1}{k_n} + \frac{2I_2}{k_n} - \frac{4}{k_n} \sqrt{I_1 I_2}$$

$$V_{DM}^2 = \frac{2}{k_n} (I_1 + I_2) - \frac{4}{k_n} \sqrt{\left( I + \frac{\Delta I}{2} \right) \left( I - \frac{\Delta I}{2} \right)}$$

$$\frac{k_n}{4} V_{DM}^2 = I - \sqrt{I^2 - \left( \frac{\Delta I}{2} \right)^2}$$

Rearrange

$$\sqrt{I^2 - \left( \frac{\Delta I}{2} \right)^2} = I - \frac{k_n}{4} V_{DM}^2 \quad \text{Square both sides}$$

$$I^2 - \left( \frac{\Delta I}{2} \right)^2 = I^2 - \frac{k_n}{2} I V_{DM}^2 + \frac{k_n^2}{16} V_{DM}^4$$

$$\frac{\Delta I^2}{4} = \frac{k_n}{2} I V_{DM}^2 - \frac{k_n^2}{16} V_{DM}^4$$

$$\Delta I^2 = 2k_n I V_{DM}^2 - \frac{k_n^2}{4} V_{DM}^4$$

$$\Delta I^2 = \frac{k_n^2}{4} V_{DM}^2 \left[ \frac{2k_n I \cdot 4}{k_n^2} - V_{DM}^2 \right]$$

$$\Delta I = \frac{k_n}{2} V_{DM} \sqrt{\frac{8I}{k_n} - V_{DM}^2}$$

valid

$$-\sqrt{\frac{8I}{k_n}} \leq V_{DM} \leq \sqrt{\frac{8I}{k_n}}$$

When current completely switches to one side  $\rightarrow V_{DM} = V_{max}$

$$V_{DM} = V_{max} \quad \Delta I = 2I$$

$$2I = \Delta I = \frac{k_n}{2} V_{max} \sqrt{\frac{8I}{k_n} - V_{max}^2} \rightarrow \text{Solve} \rightarrow V_{max} = \sqrt{\frac{4I}{k_n}}$$

$$\Delta I = \frac{k_n}{2} V_{DM} \sqrt{\frac{8I}{k_n} - V_{DM}^2}$$

$$\downarrow$$


$$V_{max}^2 = \frac{4I}{k_n}$$

$$= \frac{4I}{2 \cdot V_{max}^2} \cdot V_{DM} \cdot \sqrt{2V_{max}^2 - V_{DM}^2}$$

$$\text{sub.} \quad k_n = \frac{4I}{V_{max}^2}$$

$$= \frac{2I}{V_{max}^2} \times V_{DM} \cdot \sqrt{2} V_{max} \sqrt{1 - \frac{1}{2} \left( \frac{V_{DM}}{V_{max}} \right)^2}$$
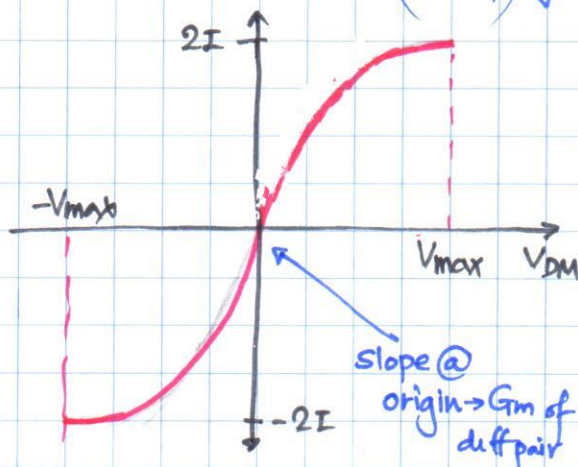
$$\Delta I = 2\sqrt{2} I \left( \frac{V_{DM}}{V_{max}} \right) \sqrt{1 - \frac{1}{2} \left( \frac{V_{DM}}{V_{max}} \right)^2}$$



\* In bipolar case as  $V_{DM} \uparrow$   
 $\Delta I$  approaches  $2I$  asymptotically.

\* In MOSFET case @  $V_{DM} = V_{max}$   
 $\Delta I = 2I$ .

\* Key point: one of the MOSFET  
 turns off  
 ( $V_{GS} = V_{TH}$ )

$$\text{@ } V_{DM} = 0 \Rightarrow I_1 = I_2 = I = \frac{k_n}{2} (V_{GS} - V_{TH})^2 = \frac{k_n}{2} V_{Dsat}^2$$

$$V_{Dsat} = \sqrt{\frac{2I}{k_n}} \Rightarrow V_{max} = \sqrt{\frac{4I}{k_n}} = \sqrt{2} V_{Dsat}$$

If  $V_{Dsat} = 200\text{mV} \rightarrow V_{max} = 283\text{mV}$   $\leftarrow$   
 current switched completely

$$\Delta I = 2\sqrt{2} I \left( \frac{V_{DM}}{V_{max}} \right) \sqrt{1 - \frac{1}{2} \left( \frac{V_{DM}}{V_{max}} \right)^2}$$

for  $\frac{V_{DM}}{V_{max}} \ll 1$

$$\Delta I \approx 2\sqrt{2} I \left( \frac{V_{DM}}{V_{max}} \right)$$

$$\frac{\Delta I}{V_{DM}} \approx \frac{2\sqrt{2} I}{V_{max}} = \frac{2\sqrt{2} I}{\sqrt{4I}} \cdot \sqrt{K_n} = \sqrt{2} \sqrt{I} \sqrt{K_n}$$

$$= \sqrt{2 K_n I} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I}$$

$\nearrow$   
Cm of diff pair

$\uparrow$   
gm of Each transistor