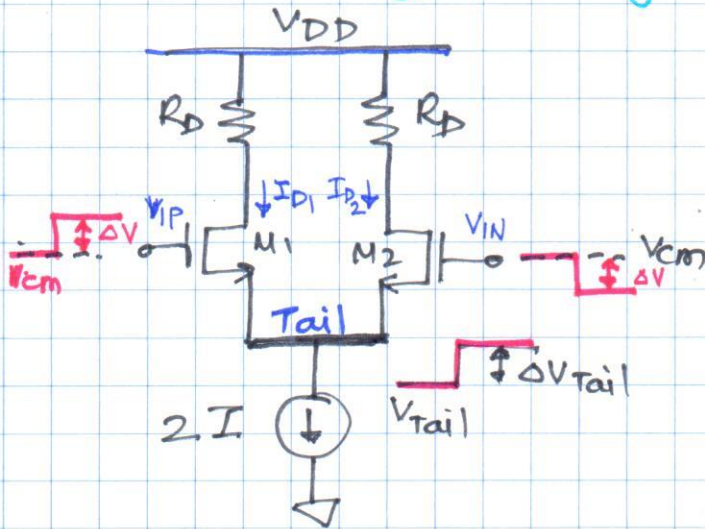


27MAR2020

Concept of virtual ground @ tail.



Zoom in around $V_{IP} - V_{IN} = 0$
 Orig. $V_{IP} = V_{IN} = V_{cm}$.
 Now apply $\Delta V \uparrow$ to V_{IP}
 $\Delta V \downarrow$ to V_{IN}

assume V_{tail} changes to $V_{tail} + \Delta V_{tail}$

Since $I_{D1} + I_{D2} = 2I$

$$I_{D1} = I + \Delta I$$

$$I_{D2} = I - \Delta I$$

Transistors M_1 & M_2 behave like transconductors (ignoring r_o)

$$\Delta I_{D1} = \Delta I = g_{m1}(\Delta V_{IP} - \Delta V_{tail})$$

$$= g_{m1}(\Delta V - \Delta V_{tail})$$

$$\Delta I_{D2} = -\Delta I = g_{m2}(\Delta V_{IN} - \Delta V_{tail})$$

$$= g_{m2}(-\Delta V - \Delta V_{tail})$$


M_1 & M_2 identical $g_{m1} = g_{m2} = g_m$

$$g_m(\Delta V - \Delta V_{tail}) = -g_m(-\Delta V - \Delta V_{tail})$$

$$\Rightarrow \Delta V_{tail} = 0$$




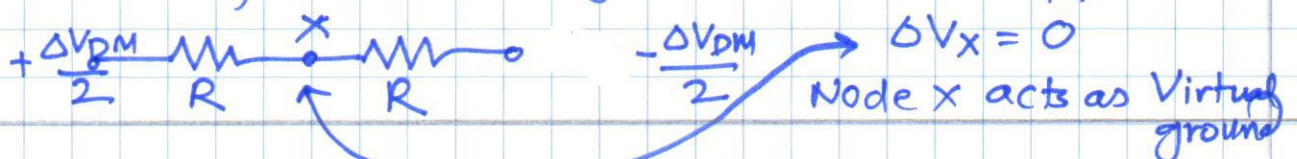Hence "Tail" node acts like virtual ground "for small signal differential i/ps"




Same analysis is valid for BJT diff pair.

Half circuit Concept

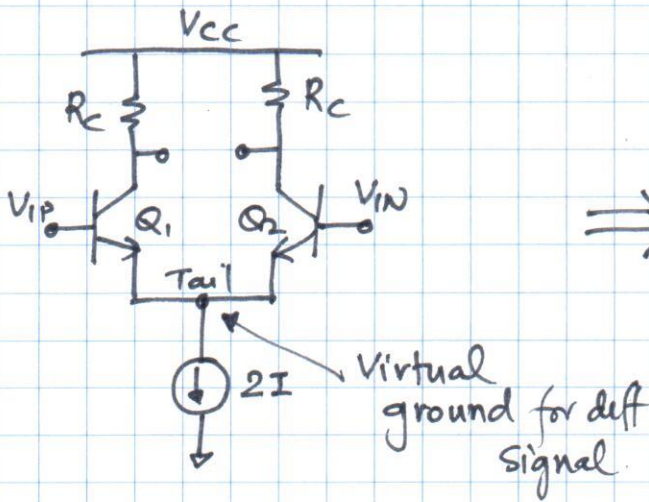

⇒

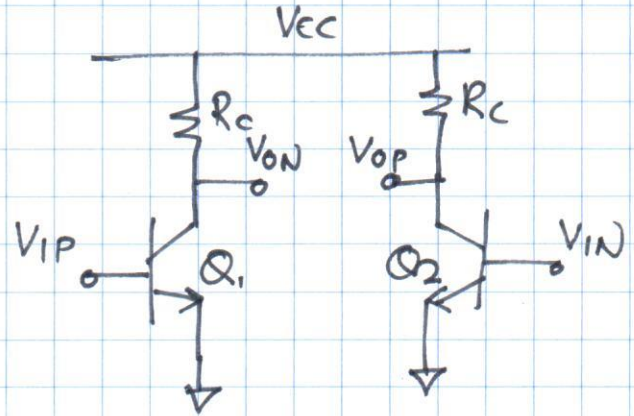

$$V_{ON} = -g_m R_c V_{IP} = -g_m R_c \frac{\Delta V_{DM}}{2}$$

$$V_{OP} = -g_m R_c V_{IN} = -g_m R_c \left(\frac{-\Delta V_{DM}}{2} \right)$$


$$(V_{OP} - V_{ON}) = g_m R_c (V_{IP} - V_{IN})$$

Diff pair - diff voltage gain = $\frac{V_{OP} - V_{ON}}{V_{IP} - V_{IN}} = g_m R_c$

* g_m - Transconductance for each transistor

$$g_m = \frac{I}{V_T}$$

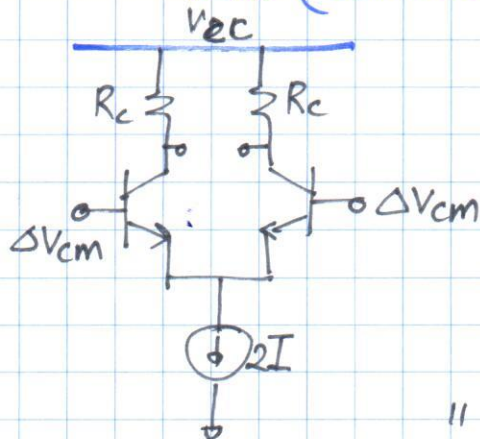* What happens when V_{cm} (common-mode) i/p voltage changes?



for ΔV_{cm} @ both V_{IP} & V_{IN}


$$V_{OP} = V_{ON} = V_{CC} - I R_c$$

NO CHANGE

$$\text{common mode gain} = 0$$

" ASSUMING CURRENT SOURCE IS IDEAL "

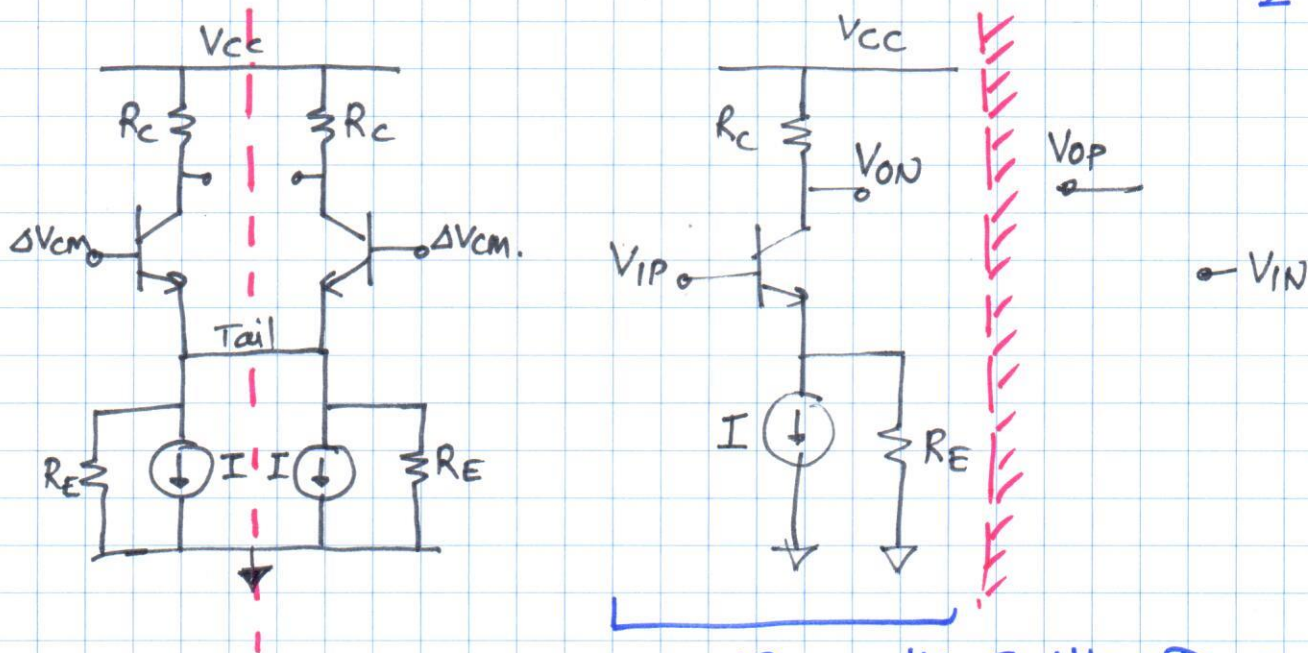Consider current source ^(2I) with o/p resistance $\frac{R_E}{2}$



CE amplifier with Emitter Degon. (LIB - page 1)

$$\frac{V_{ocm}}{V_{icm}} = \text{Common-mode gain} = - \frac{g_m}{1 + g_m R_E} R_c$$

Effective g_m .

Current source - large $R_E \rightarrow g_m R_E \gg 1$

$$\frac{V_{ocm}}{V_{icm}} \approx - \frac{g_m}{g_m R_E} \cdot R_c = - \frac{R_c}{R_E}$$

If Quality of current source is good

" R_E very large"


then $\left| \frac{V_{ocm}}{V_{icm}} \right| \ll 1$

This is the reason we were trying to get current sources with high output R_o "cascode mirrors"

★ Identical analysis is applicable to MOS Diff Pair Amplifier.

Concept Common-mode Rejection Ratio (CMRR)

(Diff in Single Ended O/p)

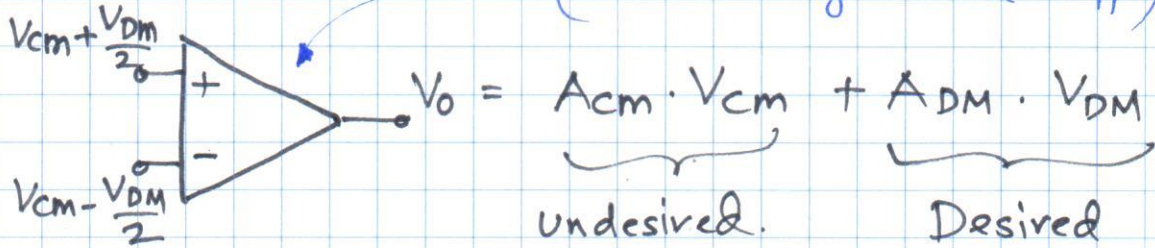


$$CMRR = 20 \log \left| \frac{A_{DM}}{A_{CM}} \right|$$

"Ability to reject common-mode signals"

* Remember ECG example 50 Hz HUM.

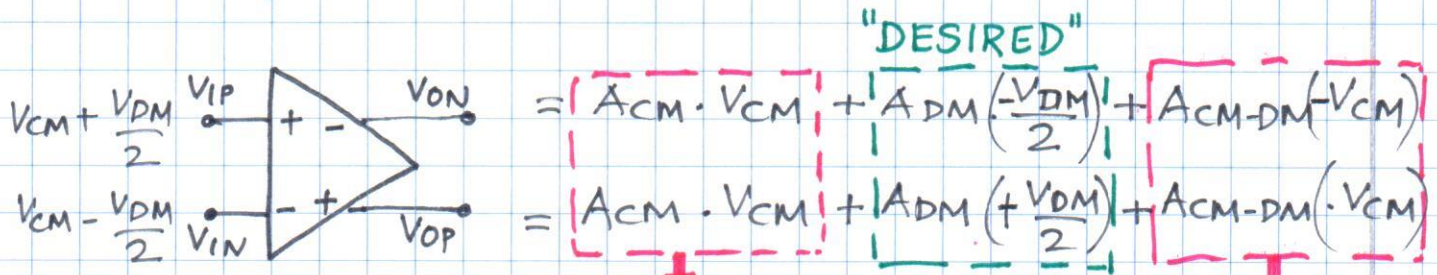For amplifier with "Differential Outputs" →




- Rejected by next diff amp.
- Changes bias point
— may impact small sig. gain
- Can limit o/p voltage swing

ACM-DM - Common-Mode to Diff-Mode Conversion

- Corrupts desired differential signal
- Can't be removed by next diff. amplifiers
- Due to circuit asymmetry due to "MISMATCHES"

CMRR Examples

Single-Ended Output

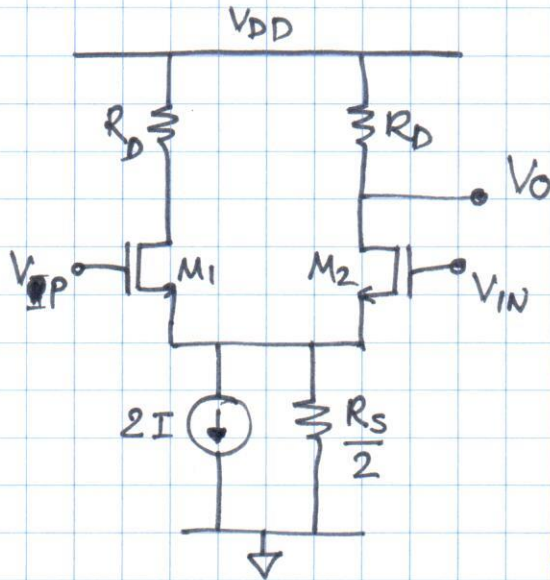

Note: we are only looking @ one o/p.

$$|A_{DM}| = \frac{g_m R_D}{2}$$


← Since we are looking at one side only.

$$|A_{CM}| = \frac{R_D}{R_S}$$

$$CMRR = 20 \log \left| \frac{A_D}{A_{CM}} \right| = 20 \log \left(\frac{g_m R_D}{2} \cdot \frac{R_S}{R_D} \right)$$

$$CMRR = 20 \log \left(\frac{g_m \cdot R_S}{2} \right)$$

Differential output

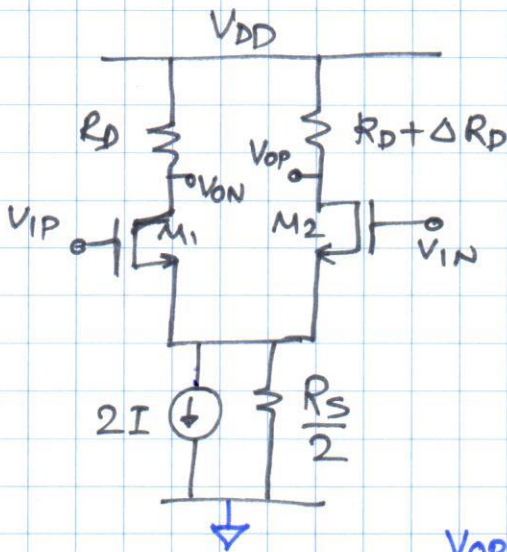

Consider only mismatch due to o/p resistor, (all other identical)

For common-mode i/p V_{CM} to both sides

$$\frac{V_{O1}}{V_{IP_{CM}}} = \frac{V_{O2}}{V_{CM}} = - \frac{R_D}{R_S}$$

$$\frac{V_{O2}}{V_{IN_{CM}}} = \frac{V_{O1}}{V_{CM}} = - \frac{R_D + \Delta R_D}{R_S}$$


$$\frac{V_{O2} - V_{O1}}{V_{CM}} = - \frac{\Delta R_D}{R_S} = A_{CM-DM}$$

Common-mode to differential mode.

$$CMRR = 20 \log \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

$$= 20 \log \left| \frac{g_m R_D}{\Delta R_D / R_S} \right|$$

$$= 20 \log \left| \frac{g_m R_S}{\Delta R_D / R_D} \right|$$

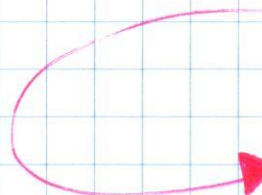
 CMRR very high for Fully Differential circuit

$\frac{\Delta R_D}{R_D} \rightarrow$ degree of Matching

$\rightarrow < 1\%$ easily achievable.

☆ You need to take into account mismatches due to other components as well (transistors)